


Guest Lectures for Dr. MacFarlane's EE3350

Michael Plante

Sat., 11-08-2008

Write name in corner.

1. Problem Statement

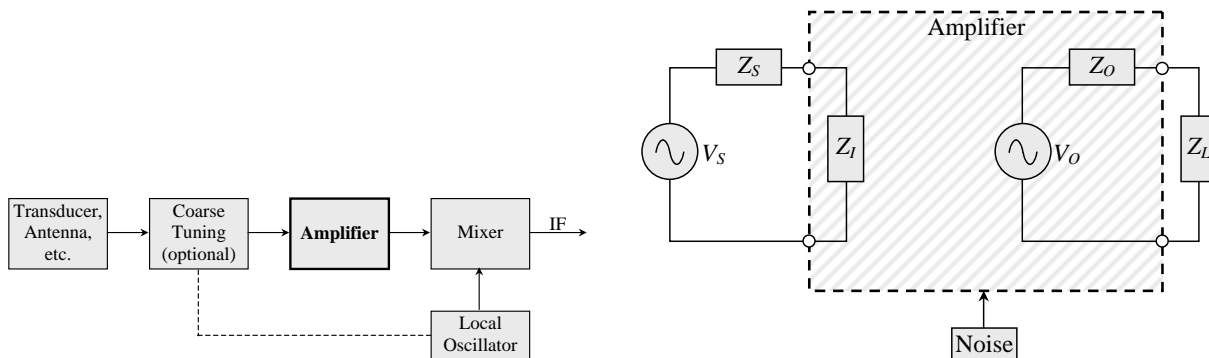

- Formulas simplified, not applicable at RF
- *Noise Factor* given by:

$$F_0 = \frac{(\text{noise total @ output})}{(\text{noise from src @ output})} = 1 + \frac{(\text{noise from amp @ output})}{(\text{noise from src @ output})}$$


- Can be rewritten as:

$$F_0 = \frac{(\text{noise tot @ out})}{(\text{gain})(\text{src noise @ inp})} = \frac{(\text{noise tot @ out})}{(\text{gain})(\text{src noise @ inp})} \frac{(\text{sig @ inp})}{(\text{sig @ out})} = \frac{(\text{SNR})_{\text{in}}}{(\text{SNR})_{\text{out}}} > 1$$

- Will use previous formula here, but latter formula useful for nonlinear systems
- Measures noisiness of amp, *relative* to source noise
- *Noise Figure* — $NF = 10 \log_{10} F_0 > 0$ (dB)


2. Superposition Review

- Short voltage, Open current

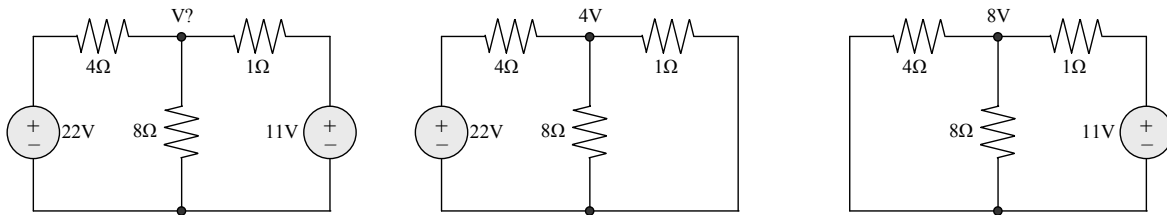

- We'll add RMS² output noise voltages


3. PSD Primer

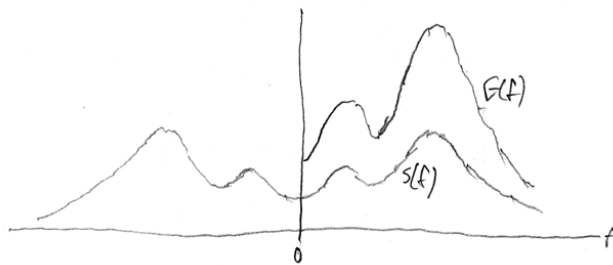

Bendat and Piersol p. 131

$$S_{xx}(f) = \int_{-\infty}^{\infty} R_{xx}(\tau) e^{-j2\pi f\tau} d\tau \quad G_{xx}(f) = 2S_{xx}(f)$$

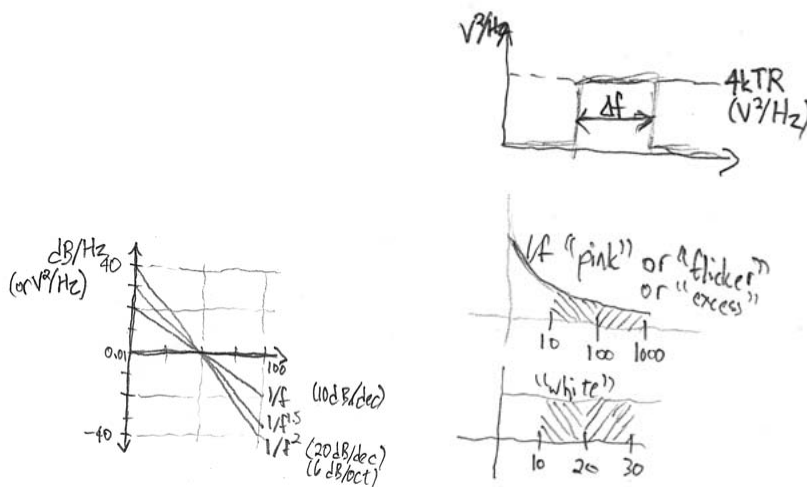- FT of autocorrelation; used for random signals, while FT of signal itself used for deterministic signals
- We will use one-sided PSD here, as that is more common; 2-sided is half as large



$$20 \log_{10} \frac{V}{V_0} = 10 \log_{10} \frac{V^2}{V_0^2}$$

$$\text{area} = 4kTR \Delta f \quad (\text{V}^2)$$


$$V_{\text{RMS}} = \sqrt{\text{area}} = \sqrt{4kTR \Delta f}$$

$$\text{area} = 4kT \Delta f / R \quad (\text{A}^2)$$

- talk dB/dec

- talk equal power per linear range or per decade/octave
- Johnson noise (WGN), $k \approx 1.38 \times 10^{-23} \text{ J/K}$, $k \approx 4 \times 10^{-21} \text{ J}$ @289.9 K or 62.2 °F
- $1/f$ and $|H(\omega)|^2$ (Bode/Controls), origin annoyance, just use it
- Shot noise from discrete events (photons/electrons), rain on tin roof, white, area = $2qI\Delta f$ (A²)
- Reduced by metal film resistors and some types of feedback, not covered
- $q \approx 1.602 \times 10^{-19} \text{ C}$, shot: $1 \text{ mA}_{\text{DC}} \Rightarrow 17.90 \text{ pA}/\sqrt{\text{Hz}}$, Johnson: 62.5Ω @289.9 K $\Rightarrow 1 \text{ nV}/\sqrt{\text{Hz}}$
- Hit flicker, popcorn, avalanche

4. Nonideal Op Amp Primer

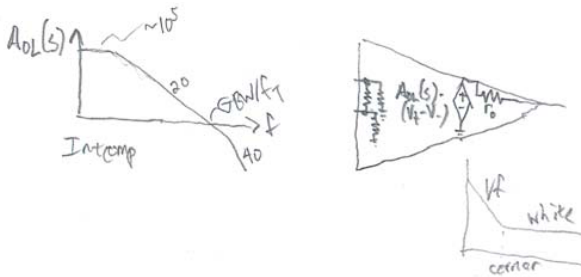

- Harry Black, 1927 negative feedback amp, 1934 paper, 1937 patent, permitted operational amplifiers, used in analog computers
- Talk input Z, gain, dominant pole, second pole, output resistance, internal compensation

- Talk about $1/f$, white, averaging operation to get effective noise
- Mention stability and second pole
- Mention ideal op-amp problem (equal V, 0 I), and the fact that another problem will come up
- Draw (not shown separately here) noisy ideal opamp, talk noise src dominance


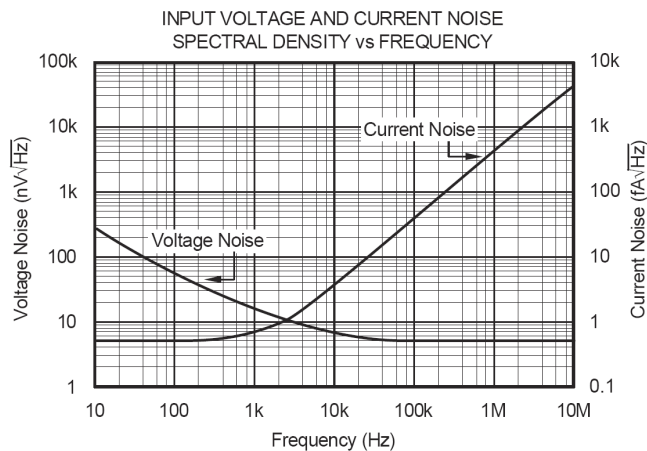


Figure 4.1: Noise in TI/BB OPA2350

- Good GP op-amp, chose arbitrary BW of 180 kHz to 220 kHz, meaning $\Delta f = 40000$ Hz
- $e_n = 5 \text{ nV}/\sqrt{\text{Hz}}$ or $e_{n'} = 1 \mu\text{V}_{\text{RMS}}$
- Fit from 10k to 10MHz gives $i_n(f) \approx f/2500 \text{ fA}/\sqrt{\text{Hz}}$

$$i_n \rightarrow \sqrt{\frac{1}{40000} \int_{180000}^{220000} \frac{f^2}{2500^2} df} \approx 80 \text{ fA}/\sqrt{\text{Hz}} \text{ or } i_{n'} = 16 \text{ pA}_{\text{RMS}}$$

5. Inverting Operational Amplifier

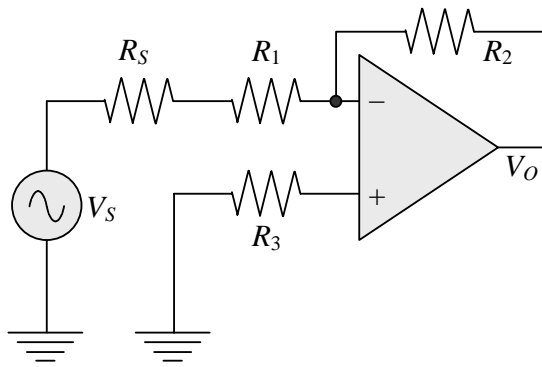

- Define $R'_1 = R_1 + R_S$. Choice of R_3 as either R_2 in parallel with R'_1 or as zero. Talk bias I.
- $R_S = 75 \text{ k}$, $R_1 = 75 \text{ k}$, $R_2 = 300 \text{ k}$, $R_3 = 100 \text{ k}$, $R'_1 = 150 \text{ k}$
- V_S , e_{R_S} , and e_{R_1} all see the same gain; e_{R_3} , e_n , and $i_{np}R_3$ all see the same gain.

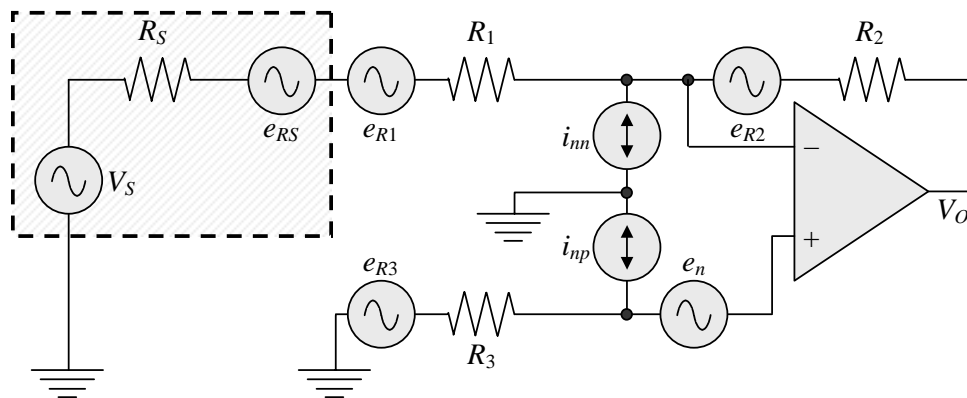


Figure 5.1: Noise Sources in Inverting Operational Amplifier

Source	Node Voltage	RMS	Noise (μV^2)
R_S		$e_{rs}R_2/R'_1$	192
R_1		$e_{r1}R_2/R'_1$	192
R_2		e_{r2}	192
R_3	$\frac{e_{r3}}{R'_1} = \frac{v_O - e_{r3}}{R_2}$	$e_{r3} (1 + R_2/R'_1)$	576
$e_{n'}$		$e_{n'} (1 + R_2/R'_1)$	9
i_{nn}	$i_{nn} + \frac{0 - v_O}{R_2} = 0$	$i_{nn}R_2$	23.04
i_{np}		$i_{np}R_3 (1 + R_2/R'_1) = i_{np}R_2$	23.04

- Noise from amp at output:

$$\begin{aligned} & \frac{1}{R_1'^2} \left[e_{r1}^2 R_2^2 + e_{r2}^2 R_1'^2 + e_{r3}^2 (R_1' + R_2)^2 + e_{n'}^2 (R_1' + R_2)^2 + i_{nn}^2 R_2^2 R_1'^2 + i_{np}^2 R_2^2 R_1'^2 \right] \\ &= \frac{1}{R_1'^2} \left[4kT \Delta f (R_1 R_2^2 + R_2 R_1'^2 + R_1' R_2 (R_1' + R_2)) + e_{n'}^2 (R_1' + R_2)^2 + i_{nn}^2 R_2^2 R_1'^2 + i_{np}^2 R_2^2 R_1'^2 \right] \end{aligned}$$

- Noise from src at output:

$$\frac{1}{R_1'^2} [4kT \Delta f R_S R_2^2]$$

- Johnson noise from amp is $960 \mu\text{V}^2$ at output
- Other noise from amp is $55.08 \mu\text{V}^2$ at output
- Johnson noise from src is $192 \mu\text{V}^2$ at output
- $F_0 = 1 + 5 + \frac{459}{1600} \approx 6.3$ or $NF \approx 10 \log_{10} 6.3 \approx 8.0 \text{ dB}$

6. Instrumentation Amplifier

- Talk CMRR (50-60 dB @ 200kHz) and high input Z (10 T Ω)

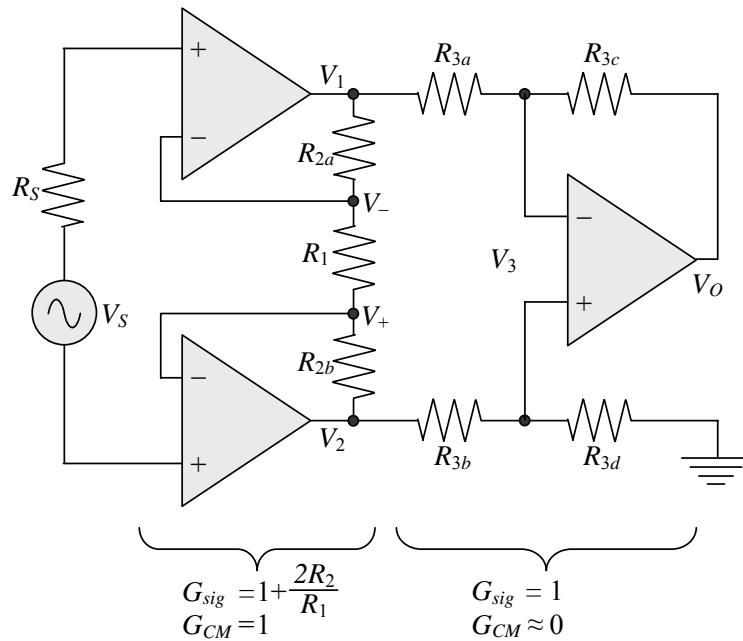


Figure 6.1: Noiseless Instrumentation Amplifier

- $v_O - v_3 = v_3 - v_1$ and $-v_3 = v_3 - v_2$ give $v_O = v_2 - v_1$, so the difference propagates with unity gain through the final stage and the common mode signal is greatly attenuated.


- In the first stage:

$$\frac{v_1 - v_-}{R_2} = \frac{v_- - v_+}{R_1} = \frac{v_+ - v_2}{R_2}$$

- Solving:


$$v_1 = \frac{(R_1 + R_2)v_- - R_2v_+}{R_1}, \quad v_2 = \frac{(R_1 + R_2)v_+ - R_2v_-}{R_1}, \quad v_2 - v_1 = (v_+ - v_-) \left(1 + \frac{2R_2}{R_1}\right)$$

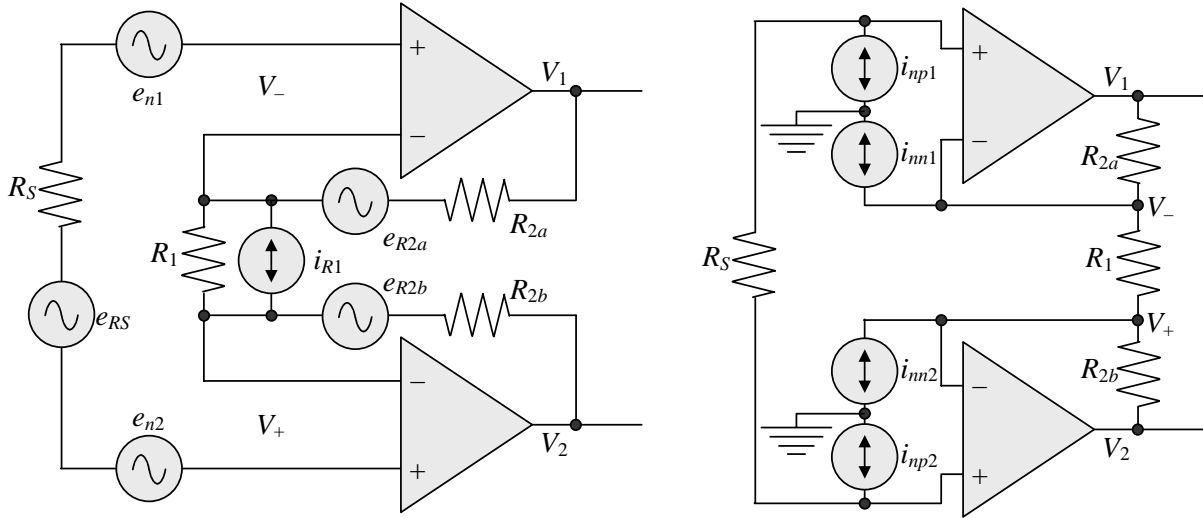- Take $R_1 = 13 \text{ k}$, $R_2 = 91 \text{ k}$, $R_S = 10 \text{ M}$, $R_3 = 10 \text{ k}$.



- e_{n1} , e_{n2} and e_{RS} all see the same gain; e_{R2a} and e_{R2b} see the same gain; i_{np1} and i_{np2} see the same gain; i_{nm1} and i_{nm2} see the same gain

Source	Node Voltage	RMS	Noise (μV^2)
R_S		$e_{RS}G$	1 440 000
e_{n1}		$e_n'G$	225
R_1	$\frac{v_1}{R_2} = i_{R1} = \frac{-v_2}{R_2}$	$2i_{R1}R_2 = e_{R1}(G - 1)$	1631
R_{2a}	$\frac{v_1 - e_{R2a}}{R_2} = 0 = \frac{-v_2}{R_2}$	e_{R2a}	58.24
i_{nm1}	$i_{nm1} - \frac{v_1}{R_2} = 0 = \frac{v_2}{R_2}$	$i_{nm}R_2$	2.120
i_{np1}	$i_{np1} = \frac{v_+ - v_-}{R_S}$	$i_{np}R_S G$	5 760 000

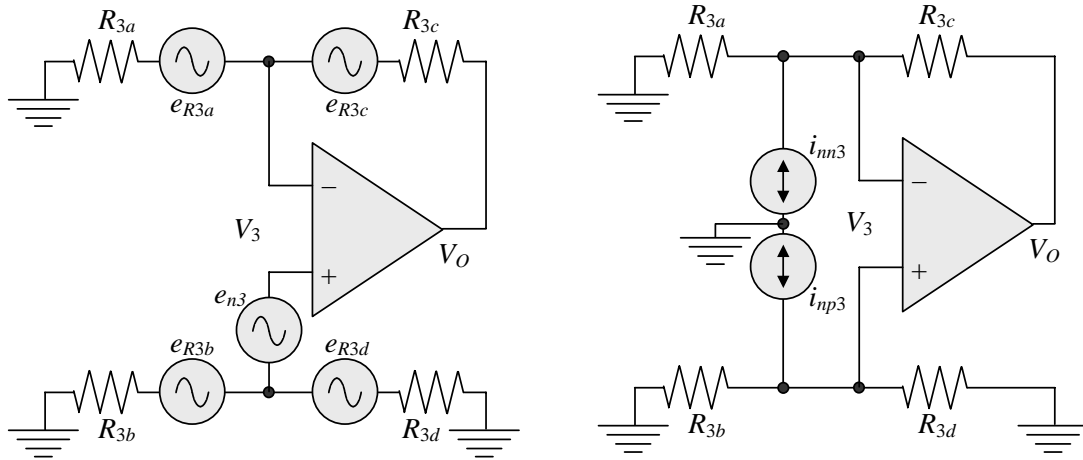

- R_{3b} and R_{3d} see the same gain.

Source	Node Voltage	RMS	Noise (μV^2)
R_{3a}	$\frac{e_{R3a}}{R_3} = \frac{-v_O}{R_3}$	e_{R3a}	6.4
R_{3b}	$\frac{e_{R3b/2}}{R_3} = \frac{v_O - e_{R3b/2}}{R_3}$	e_{R3b}	6.4
R_{3c}	$\frac{v_O - e_{R3c}}{R_3} = 0$	e_{R3c}	6.4
e_{n3}	$\frac{e_{n3}}{R_3} = \frac{v_O - e_{n3}}{R_3}$	$2e_{n'}$	4
i_{nn3}	$i_{nn3} + \frac{-v_O}{R_3} = 0$	$i_{nn}R_3$	0.0256
i_{np3}	$\frac{i_{np3}R_{3/2}}{R_3} = \frac{v_O - i_{np3}R_{3/2}}{R_3}$	$i_{np}R_3$	0.0256

- Johnson noise due to source is $1\,440\,000\ \mu\text{V}^2$
- Johnson noise due to first stage of amp is $1747\ \mu\text{V}^2$
- Opamp noise in first stage is $11\,520\,500\ \mu\text{V}^2$
- Johnson noise due to second stage of amp is $25.6\ \mu\text{V}^2$
- Opamp noise in second stage is $4.05\ \mu\text{V}^2$
- Noise Factor, with current noise on first stage broken off separately:

$$F_0 \approx 1 + 0.001549 + 8 = 9.001549, \quad NF \approx 10 \log_{10} 9.001549 \approx 9.54 \text{ dB}$$

- At very high source impedances, opamp current noise “dominates”.

7. Loose Ends

- Draw a string of single-wire amps with G,F written in. Friis:

$$F_{1,2} = F_1 + \frac{F_2 - 1}{G_1}$$

$$F_{1,2,3} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$

...

References:

- SLOD006B Op Amps for Everyone
- SLVA043B Noise Analysis in Operational Amplifier Circuits
- Bendat and Piersol — Random Data: Analysis and Measurement Procedures
- Davenport and Root — An Introduction to the Theory of Random Signals and Noise
- Horowitz and Hill — The Art of Electronics
- Bob Pease — Troubleshooting Analog Circuits