



# Digital Logic Circuits

- **Digital circuits make up all computers and computer systems. The operation of digital circuits is based on Boolean algebra, the mathematics of binary numbers.**
- **Boolean algebra is very simple, having only three basic functions, **AND**, **OR**, and **NOT**.**
- **These basic functions can be combined in many ways to provide all the functions required in the central processor of a digital computer.**
- **Digital circuits operate by performing Boolean operations on binary numbers (more about binary numbers in EE 2310).**

## First Boolean Function: NOT

- **NOT** is the simplest logical function: 1 input and 1 output.
- **NOT** is defined as follows: “The output  $f$  of **NOT**, given an input  $a$ , is the complement or opposite of the input.” Or :  $f = \bar{a}$
- **Since NOT can have only a 0 or 1 input, the output of NOT is the reverse, or complement, of the input.**
  - If the input of **NOT** is 1, the output is 0.
  - If the input of **NOT** is 0, the output is 1.
- The **NOT** function is called inversion, and the digital circuit which inverts is an inverter. The electronic circuit symbol for **NOT** is:



# The Truth Table

- The inverter input/output relationship, with one input and output, is easy to show.
- For complex functions, an I/O table is helpful.
- We call this a truth table, since it indicates the 1 (“true”) outputs, although it normally shows outputs for all input combinations.
- We will demonstrate some Boolean functions using truth tables.

## Boolean Function Truth Table

Input x	Input y	Output f
0	0	0
0	1	1
1	0	1
1	1	0

**Note:** This 2-input truth table shows the output  $f$  for all possible combinations of the binary inputs  $x$  and  $y$ .


# Second Boolean Function: **AND**

- **AND** has two or more inputs.
- The truth table for a two-input **AND** with inputs *a* and *b* is shown in the chart.
- **AND** is defined as follows:  $a \text{ AND } b = 1$  if and only if (iff)  $a = 1$  and  $b = 1$ .
- Mathematically, we represent “ $a \text{ AND } b$ ” as  $a \cdot b$  (an unfortunate choice).
- **AND** may have more than two inputs, i. e.:  $a \text{ AND } b \text{ AND } c \text{ AND } d$ .
- The electronic circuit symbols for 2- and 4-input **ANDs** are shown at the right.
- **Regardless of the number of inputs, the output of AND is 1 iff all inputs are 1**.


**AND Truth Table**

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1

**2-Input AND**

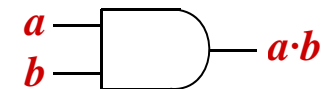

**4-Input AND**


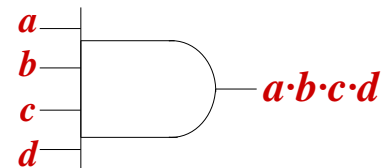


# Third Boolean Function: **OR**

- **OR** has two or more inputs.
- The **OR** truth table for two inputs  $a, b$  is shown in the adjacent chart.
- **OR** is defined as follows:  $a \text{ OR } b = 1$  if either  $a$  or  $b$  or both  $a$  and  $b = 1$ .
- Mathematically, we represent “ $a \text{ OR } b$ ” as  $a + b$  (another bad choice).
- **OR** may have more than two inputs, i. e.:  $a \text{ OR } b \text{ OR } c \text{ OR } d$ .
- The electronic circuit symbols for 2- and 4- input **ORs** are shown at the right.
- **Regardless of the number of inputs, the output of OR is 0 iff all inputs are 0.**


**OR Truth Table**

a	b	a OR b
0	0	0
0	1	1
1	0	1
1	1	1

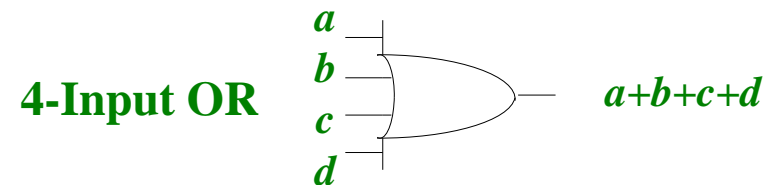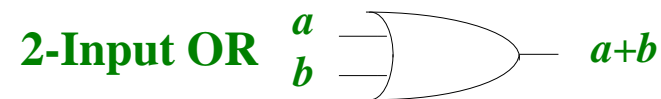
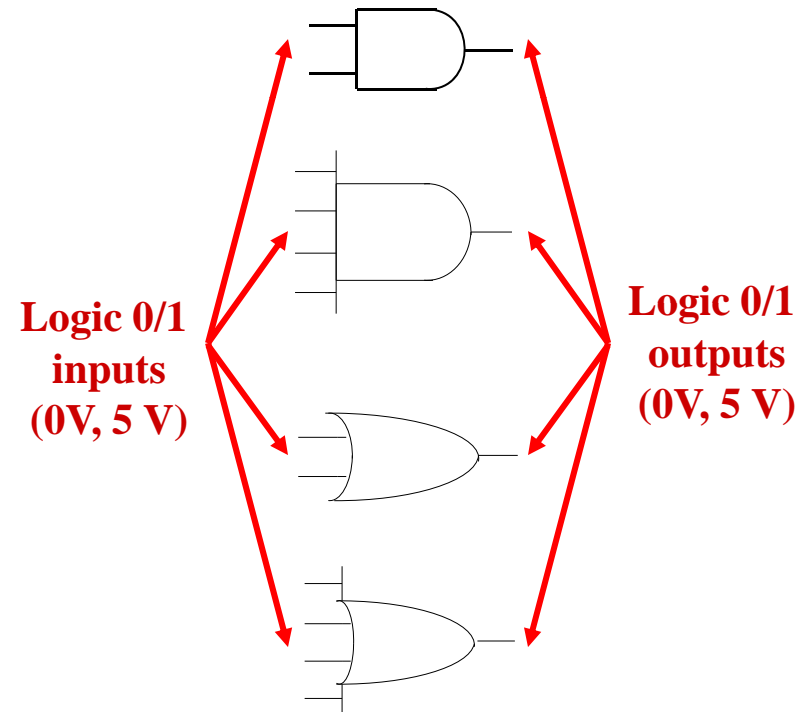
## Logic “1” and “0”

- **Electronic circuits don’t manipulate logic 1 and 0 literally.**
- **In digital circuits, the values “1” and “0” are levels of voltage, and the logic circuits that we use are technically “inverting amplifiers with saturated outputs.”**
- **In the circuits we will use, logic 0 is 0 volts, and logic 1 is 5 volts.**









## Making More Complex Boolean Functions

- The three Boolean functions discussed above can be used to form more complex functions.
- ANY computer function can be performed using combinations of **AND**, **OR**, and **NOT**.
- To simplify the definition of combinational logic (the logic of the computer CPU), any logic function can be composed of a level of **AND** gates followed by a single **OR** gate.
- There are a few other ways to form Boolean circuits, but we will cover only this one method in Lab 3.
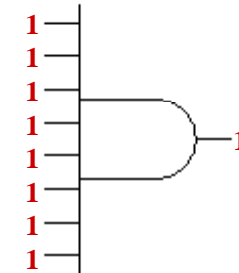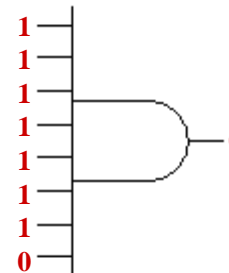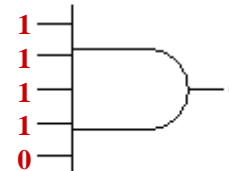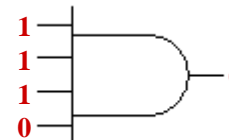
## Uniqueness of **AND**





- The uniqueness of the **AND** function is that the output of **AND** is 0 except when **EVERY** input = 1.
- In the 4 gates to the right, a SINGLE 0 input into each gate forces the output to 0.
- The output of **AND** is 1 only when ALL inputs = 1 (8-input gate to right).




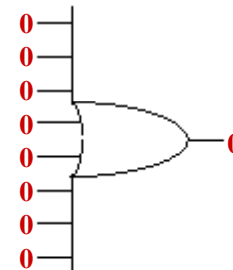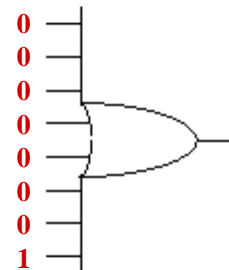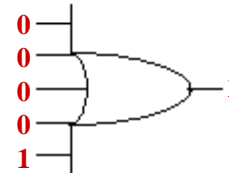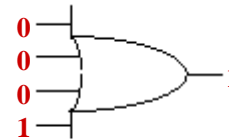
## The “Any 1” Quality of **OR**

- The output of **OR** = 1 if ANY input = 1.
- **OR** outputs a 0 iff ALL inputs = 0.
- We can use the ability of **OR** to “pass” any 1 and the unique 1- outputs of the **AND** to create Boolean functions.



# Digital Design

- In circuit design, inputs and outputs are defined by a “spec.”
- Since computer circuits use only binary numbers, inputs are always 0 and 1, and the output is always 0 and 1.
- The engineer designs the circuit between input and output by:
  - Making a truth table to represent the input/output relationship.
  - Defining a Boolean expression that satisfies the truth table.
  - Constructing a circuit that represents the Boolean function.



## Creating a Computer (“Boolean”) Function

- A “spec” for a function  $f$  of two variables  $x$  and  $y$  is that  $f = 1$  when  $x$  and  $y$  are different, and 0 otherwise.
- The truth table charts  $f$  per the “spec.”
- How can we describe this behavior with a Boolean expression?
- For the first 1, we can create an **AND** function:  $\bar{x} \cdot y$ . Note that this expression is 1 **ONLY** when  $x = 0, y = 1$ .
- For the second 1, we create  $x \cdot \bar{y}$ , which is only 1 for  $x = 1, y = 0$ .

$x$	$y$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

$\bar{x} \cdot y$        $x \cdot \bar{y}$

## Boolean Function (2)

- First 1 **AND** function:  $\bar{x} \cdot y$  .
- Second 1 **AND** function:  $x \cdot \bar{y}$  .
- The two Boolean **AND** functions each describe one of the two conditions in which  $f$  is 1.
- How do we create a Boolean function that describes BOTH conditions of  $f = 1$ ?
- Recall that any 1 is passed through **OR**.
- Then if we send both ones through a single **OR**, its output will match the specified performance of  $f$ .

$x$	$y$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

$\bar{x} \cdot y$     $x \cdot \bar{y}$


# Boolean Function (3)

- We **OR** the two **AND** functions:  

$$f = x \cdot \overline{y} + \overline{x} \cdot y$$
- We now have a complete description (Boolean expression) for the function  $f$ .
- Since we know what **AND** and **OR** circuits look like, we can build a digital circuit that produces  $f$ .

$x$	$y$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

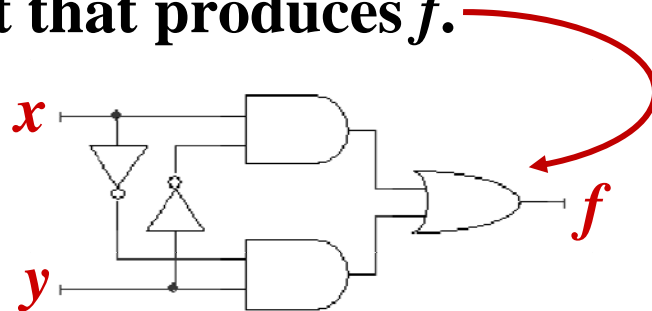$\overline{x \cdot y}$       $\overline{x \cdot y}$



# Building Boolean Functions


- As we have just seen, if we have Boolean functions that result from a truth table and “spec,” **we can convert the Boolean functions to computer circuits.**
- Consider these functions:

$$a + b + c = f$$



$$a + \bar{b} = f$$

$$(a \cdot b) + c = f$$


1:

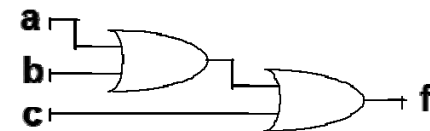

2:

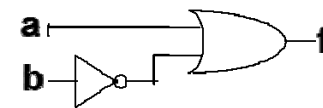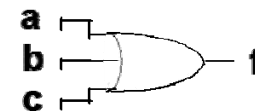

3:


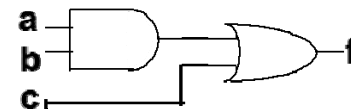


## Quick Exercise

- Designing a circuit from the Boolean expressions:

$$(a \cdot b) + (c \cdot d) = f$$

$$\bar{a} + (b \cdot c) + d = f$$

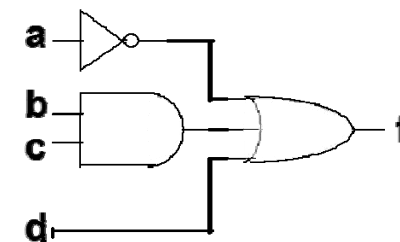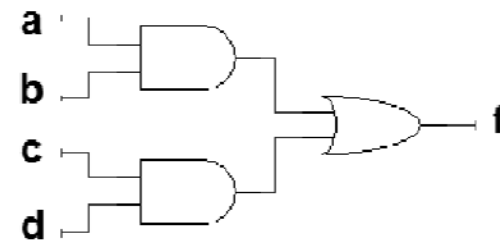

## Design: “Spec” to Truth Table to Circuit

- Say you have the following “design spec” for function  $f$ :
  - There are three inputs  $x$ ,  $y$ , and  $z$ , to a digital circuit.
  - The circuits must have an output of 1 when  $y = z = 1$  and  $x = 0$ ; and when  $x = z = 1$  and  $y = 0$ .
  - Design the circuit using **AND**, **OR**, and **NOT** gates.

$x$	$y$	$z$	$f(x, y, z)$	AND's
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$f = \bar{x}yz$
1	0	0	0	
1	0	1	1	$f = x\bar{y}z$
1	1	0	0	
1	1	1	0	

The truth table above shows the desired output:

$f = 1$  when  $x=0, y, z = 1$ ,  
 $f = 1$  when  $y=0, x, z = 1$ .



# Getting the Boolean Function



- We can create a Boolean function for each of the two “1” conditions:
  - Inverting x and ANDing it with y and z creates a 1 for the first condition.
  - Inverting y and ANDing it with x and z creates the other 1.
  - Notice that each AND function produces a 1 ONLY for that combination of variables.
- According to the definition of OR, any 1 goes through that gate.
  - Therefore OR the two AND functions together to get a function that is 1 for both cases!

<u>x</u>	<u>y</u>	<u>z</u>	f(x, y, z)	AND's
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$f = \bar{x}yz$
1	0	0	0	
1	0	1	1	$f = x\bar{y}z$
1	1	0	0	
1	1	1	0	

This is a 1 ONLY for (0,1,1)


This is a 1 ONLY for (1,0,1)

# Boolean Function and Circuit

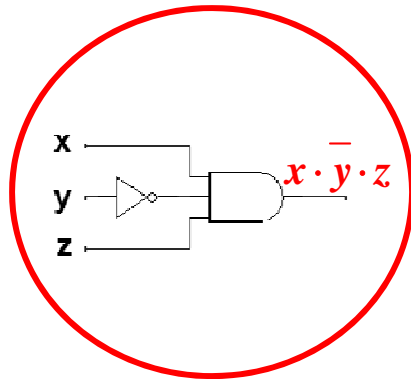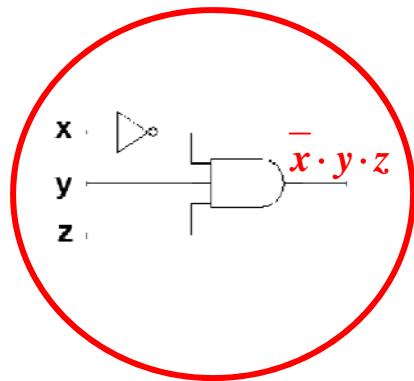


$x$	$y$	$z$	$f(x, y, z)$	AND's
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{x} \cdot y \cdot z$
1	0	0	0	
1	0	1	1	$x \cdot \bar{y} \cdot z$
1	1	0	0	
1	1	1	0	

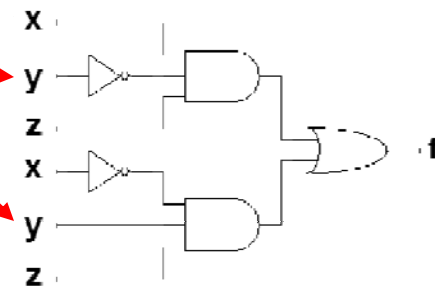The **OR** function ( $f$ ) completely satisfies the spec and truth table!


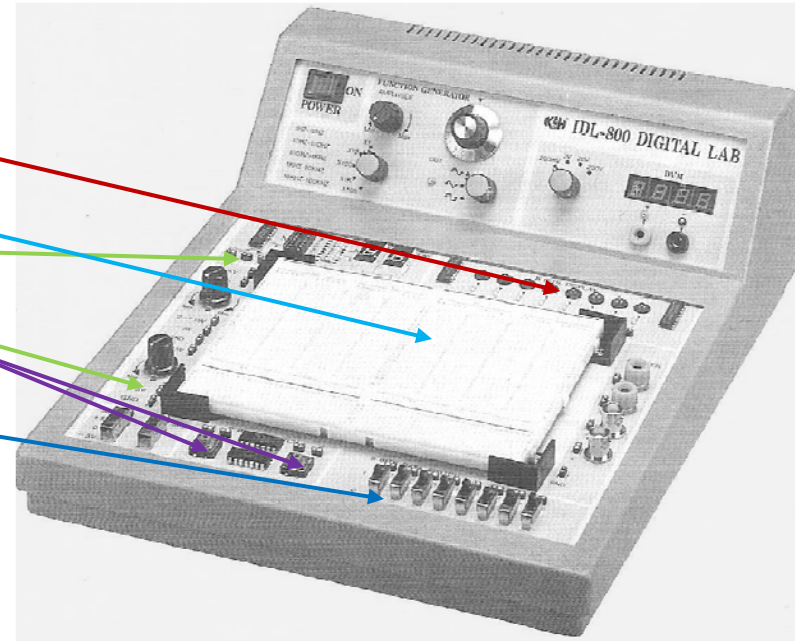
## Lab Instrument: IDL-800

- **Key parts:**
  - LED indicators
  - Circuit board
  - +5V power
  - Momentary 0-1 switches
  - 0-1 input switches



## Digital Circuit Kit

- The digital circuit kits are also used in EE 2310.
- You will only be using **AND**, **OR**, and **NOT** circuits (see below).
- **NEVER** replace a bad or broken circuit in the kit. Give to the TA to be replaced.
- **ALWAYS** put up the kit when you are done.




## Plugging in a Digital IC and Wiring Up a Circuit


- **Remember: The circuit is ALWAYS plugged in so that it spans a channel in the circuit board.**
- **Therefore a wire plugged into any of the parallel holes into which a chip leg is plugged is connected to that leg of the chip.**




# Digital IC Circuit Diagrams

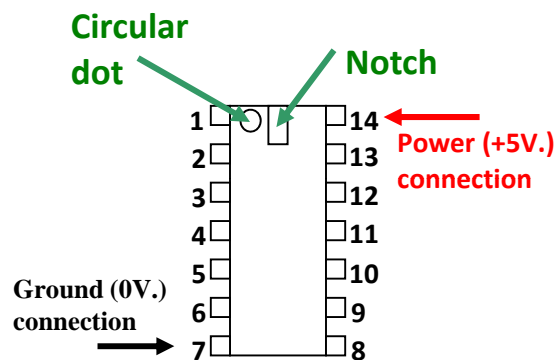


74 LS XXX Chip Outline

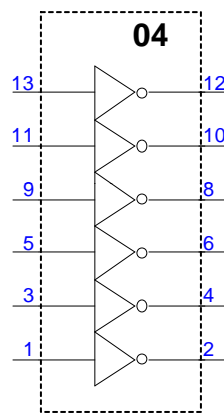

SN 74LS04 Hex inverter gate

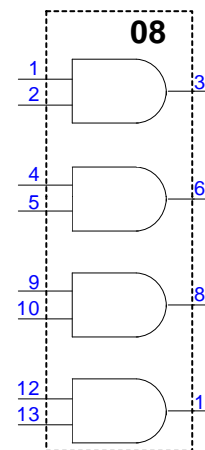

SN 74LS08 Quad 2-input AND gate

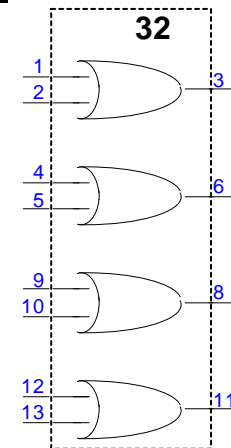

SN 74LS32 Quad 2-input OR gate

- You will be using the 74LS04, 74LS08, and 74LS32 digital integrated circuits.
- The diagram above (also in your manual) shows the outline of the chip, with power/ground inputs.
- The three chip schematics show how the circuits in each chip connect to the input pins.