




AC RL and RC Circuits

- When a sinusoidal AC voltage is applied to an RL or RC circuit, the relationship between voltage and current is altered.
- The voltage and current still have the same frequency and cosine-wave shape, but voltage and current no longer rise and fall together.
- To solve for currents in AC RL/RC circuits, we need some additional mathematical tools:
 - Using the complex plane in problem solutions.
 - Using transforms to solve for AC sinusoidal currents.

Imaginary Numbers


- Solutions to science and engineering problems often involve $\sqrt{-1}$.
- Scientists define $i = \sqrt{-1}$.
- As we EE's use i for AC current, we define $j = \sqrt{-1}$.
- Thus technically, $j = -i$, but that does not affect the math.
- Solutions that involve j are said to use “imaginary numbers.”
- Imaginary numbers can be envisioned as existing with real numbers in a two-dimensional plane called the “Complex Plane.”

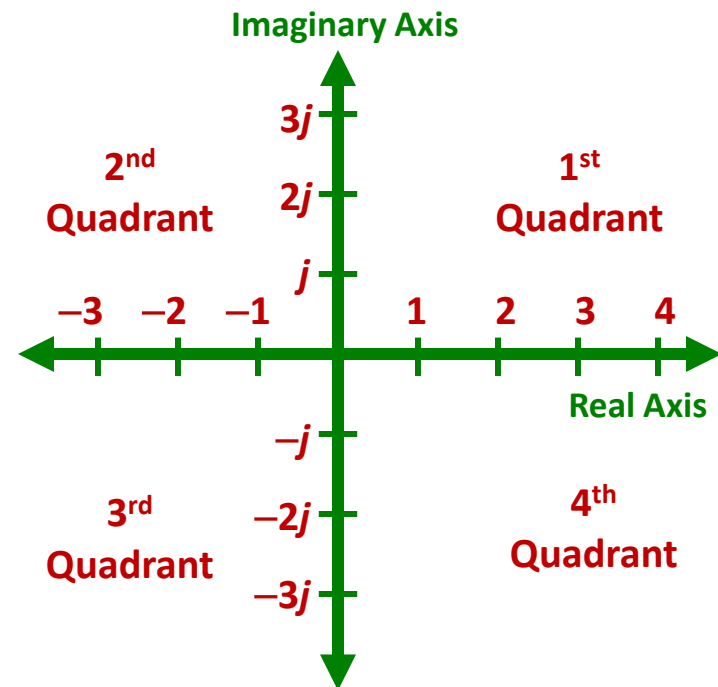


The Complex Plane

The Complex Plane

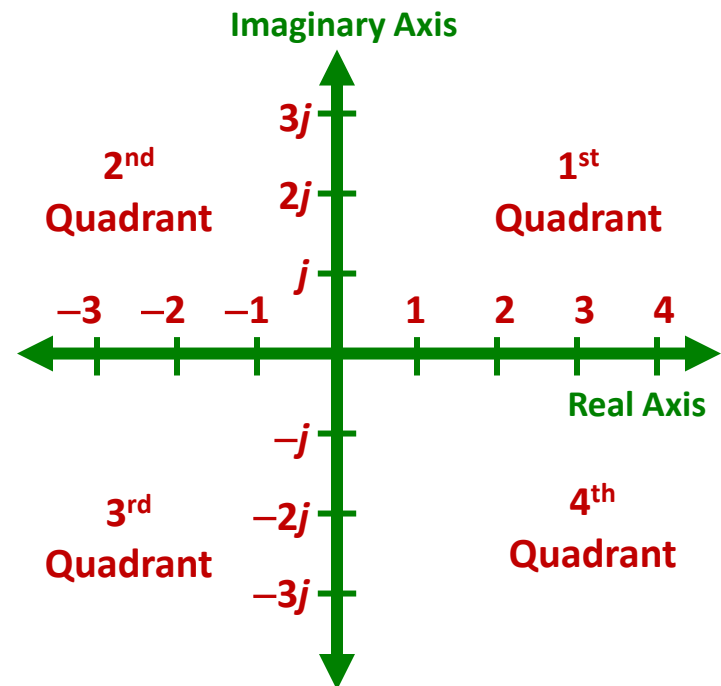- In the complex plane, imaginary numbers lie on the y-axis, real numbers on the x-axis, and complex numbers (mixed real and imaginary) lie off-axis.
- For example, 4 is on the +x axis, -8 is on the $-x$ axis, $j6$ is on the + y axis, and $-j14$ is on the $-y$ axis.
- Complex numbers like $6+j4$, or $-12-j3$ lie off-axis, the first in the first quadrant, and the second in the third quadrant.




Why Transforms?

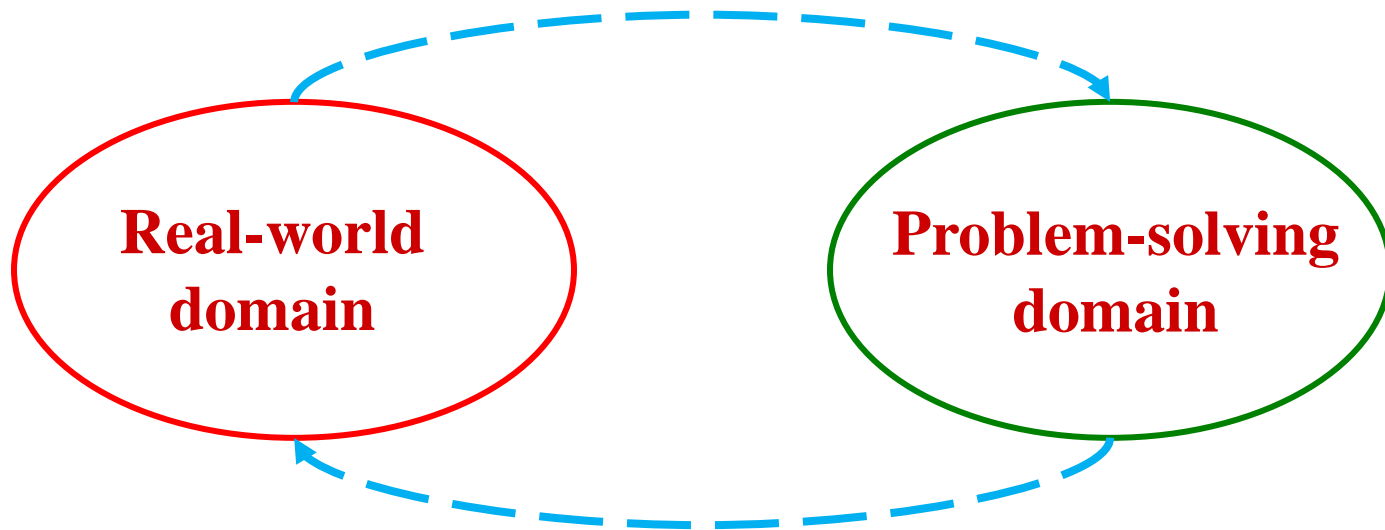

- **Transforms move a problem from the real-world domain, where it is hard to solve, to an alternate domain where the solution is easier.**
- **Sinusoidal AC problems involving R - L - C circuits are hard to solve in the “real” time domain but easier to solve in the ω -domain.**

The ω Domain

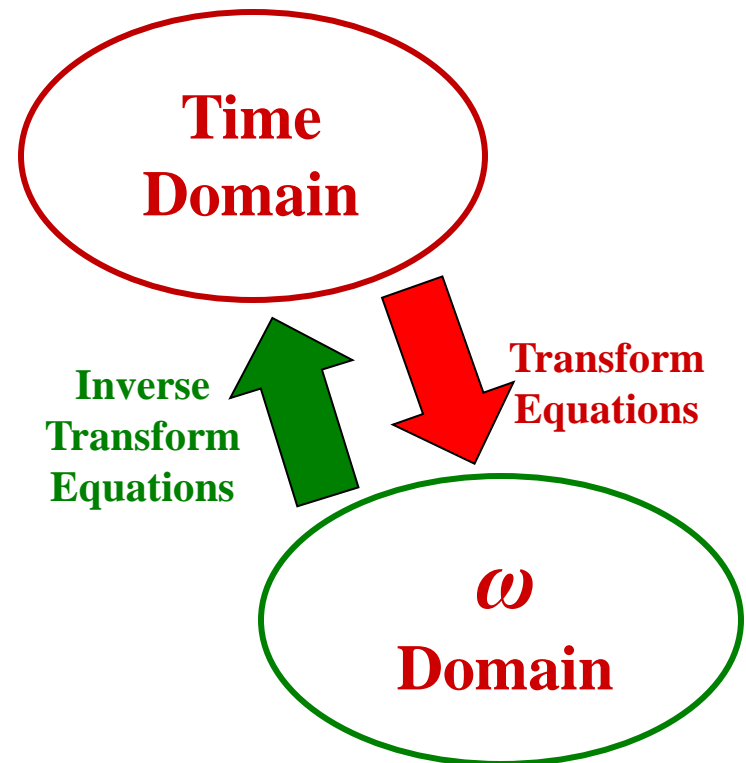- In the time domain, *RLC* circuit problems must be solved using calculus.
- However, by transforming them to the ω domain (a radian frequency domain, $\omega = 2\pi f$), the problems become algebra problems.
- A catch: We need transforms to get the problem to the ω domain, and inverse transforms to get the solutions back to the time domain!



A Review of Euler's Formula

- You should remember Euler's formula from trigonometry (if not, get out your old trig textbook and review): $e^{\pm jx} = \cos x \pm j \sin x$.
- The alternate expression for $e^{\pm jx}$ is a complex number. The real part is $\cos x$ and the imaginary part is $\pm j \sin x$.
- We can say that $\cos x = \text{Re}\{e^{\pm jx}\}$ and $\pm j \sin x = \text{Im}\{e^{\pm jx}\}$, where $\text{Re} =$ "real part" and $\text{Im} =$ "imaginary part."
- We usually express AC voltage as a cosine function. That is, an AC voltage $v(t)$ can be expressed as $v(t) = V_p \cos \omega t$, where V_p is the peak AC voltage.
- Therefore we can say that $v(t) = V_p \cos \omega t = V_p \text{Re}\{e^{\pm j\omega t}\}$. This relation is important in developing inverse transforms.

Transforms into the ω Domain

Element	Time Domain	ω Domain Transform
AC Voltage	$V_p \cos \omega t$	V_p
Resistance	R	R
Inductance	L	$j\omega L$
Capacitance	C	$1/j\omega C$

- The time-domain, sinusoidal AC voltage is normally represented as a cosine function, as shown above.
- R , L and C are in Ohms, Henrys and Farads.
- Skipping some long derivations (which you will get in EE 3301), transforms for the ω domain are shown above.
- Notice that the AC voltage ω -transform has no frequency information. However, frequency information is carried in the L and C transforms.


Comments on ω Transforms

Element	Time Domain	ω Domain Transform
AC Voltage	$V_p \cos \omega t$	V_p
Resistance	R	R
Inductance	L	$j\omega L$
Capacitance	C	$1/j\omega C$

- Because we are studying constant-frequency sinusoidal AC circuits, the ω -domain transforms are constants.
- This is a considerable advantage over the time-domain situation, where t varies constantly (which is why solving for sinusoidal currents in the time domain is a calculus problem).
- Two other items:
 - In the ω -domain, the units of R , $j\omega L$, and $1/j\omega C$ are Ohms.
 - In the ω -domain, Ohm's Law and Kirchoff's voltage and current laws still hold.

Solving for Currents in the ω Domain

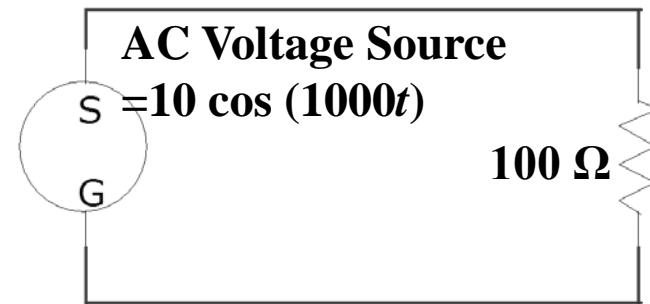- Solving problems in the frequency domain:
 - Given a circuit with the AC voltage shown, and only a resistor in the circuit, then the transform of the voltage is 10. R transforms directly as 100.
 - Solving for the circuit current, $I=V/R$, or $I=10/100 = 0.1$ A.
 - This current is the ω -domain answer. It must be inverse-transformed to the time domain to obtain a usable answer.




$$\omega\text{-domain voltage} = V_p = 10$$

$$\omega\text{-domain current} = V_p / R \\ = 10/100 = 0.1 \text{ ampere}$$

An ω Domain Solution for an L Circuit

- The ω -domain voltage is still 10.
- The ω -domain transform of $L = j\omega L = j(1000)10(10)^{-3} = j10$.
- The units of the L transform is in Ohms (Ω), i.e., the ω -domain transform of L is $j10 \Omega$.
- The value ωL is called inductive reactance (X). The quantity $j\omega L$ is called impedance (Z).
- Finding the current: $I = V/Z = 10/j10 = 1/j = -j$ (rationalizing).
- Time-domain answer in a few slides!

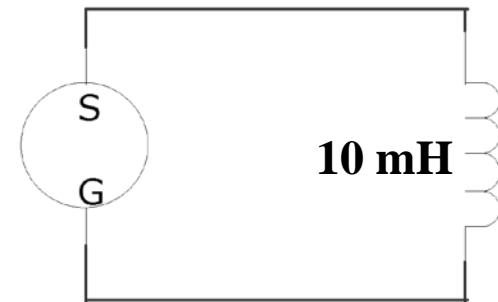


AC Voltage
 $= 10 \cos(1000t)$

ω -domain voltage = $V_p = 10$

ω -domain current = $V_p / j\omega L$
 $= 10/j10 = -j1 = -j$ ampere

An ω Domain Solution for a C Circuit

- The ω -domain voltage still = 10.
- The ω -domain transform of $C = 1/j\omega C = 1/j(1000)100(10)^{-6} = 1/j0.1 = -j10$.
- The units of the C transform is in Ohms (Ω), i.e., the ω -domain transform of C is $-j10 \Omega$.
- The value $1/\omega C$ is called capacitive reactance, and $1/j\omega C$ is also called impedance (here, capacitive impedance).
- Finding the current: $I = V/Z = 10/-j10 = 1/-j = j1$ (rationalizing) = j .
- Time-domain answer coming up!

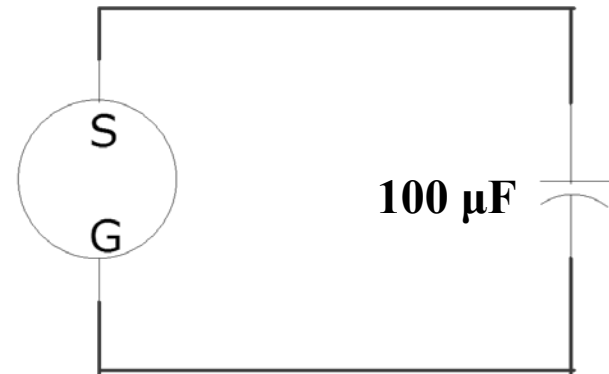


AC Voltage
= $10 \cos(1000t)$

ω -domain voltage = $V_p = 10$

ω -domain current = $V_p / (1/j\omega C)$
= $10/-j10 = j1 = j$ amperes

An *RL* ω -Domain Solution

- The ω -domain voltage still = 10.
- The ω -domain impedance is $10+j10$.
- Resistance is still called resistance in the ω -domain. The R and L transforms are called impedance, and a combination of resistance and imaginary impedances is also called impedance.
- Note: all series impedances add directly in the ω -domain.
- Finding the current: $I = V/Z = 10/(10+j10) = (\text{rationalizing}) (100-j100)/200 = 0.5-j0.5$.
- Time-domain answers next!

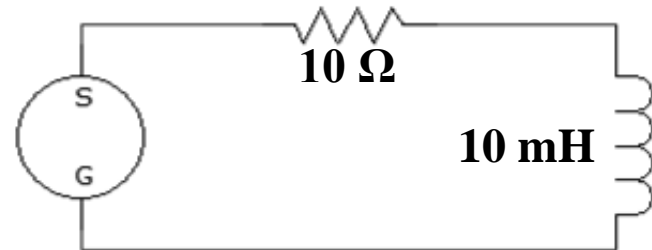

AC Voltage
= $10 \cos(1000t)$

$$\omega\text{-domain voltage} = V_p = 10$$

$$\omega\text{-domain current} = V_p / (R+j\omega L) \\ = 10 / (10+j10) = 0.5-j0.5 \text{ ampere}$$




Inverse Transforms

- Our ω -domain solutions do us no good, since we are inhabitants of the time domain.
- We required a methodology for inverse transforms, mathematical expressions that can convert the frequency domain currents we have produced into their time-domain counterparts.
- It turns out that there is a fairly straightforward inverse transform methodology which we can employ.
- First, some preliminary considerations.

Cartesian-to-Polar Transformations

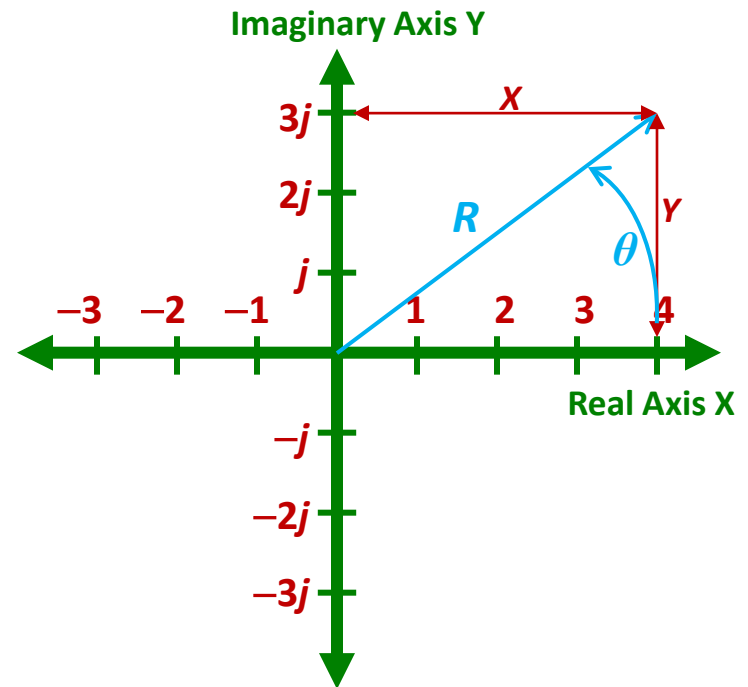
- Our ω -domain answers are complex numbers – currents expressed in the X - Y coordinates of the complex plane.
- Coordinates in a two-dimensional plane may also be expressed in R - θ coordinates: a radius length R plus a counterclockwise angle θ from the positive X -axis (at right).
- That is, there is a coordinate R, θ that can express an equivalent position to an X, Y coordinate.



Cartesian-to-Polar Transformations (2)


- The R, θ coordinate is equivalent to the X, Y coordinate if $\theta = \arctan(Y/X)$ and $R = \sqrt{X^2 + Y^2}$.
- In our X - Y plane, the X axis is the real axis, and the Y axis is the imaginary axis. Thus the coordinates of a point in the complex plane with (for example) X coordinate A and Y coordinate $+B$ is $A+jB$.
- Now, remember Euler's formula:

$$e^{\pm jx} = \cos x \pm j \sin x$$

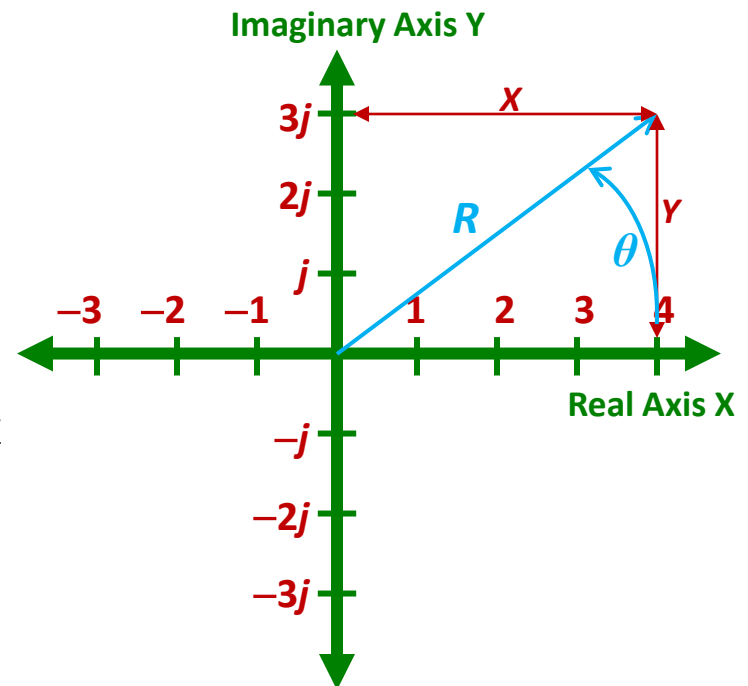

Cartesian-to-Polar Transformations (3)

- If $e^{\pm jx} = \cos x \pm j \sin x$, then $Re^{\pm jx} = R \cos x \pm Rj \sin x$.
- But in our figure, $R \cos \theta = X$, and $R \sin \theta = Y$.
- Or, $Re^{\pm j\theta} = X \pm jY$!
- What this says is that when we convert our ω -domain AC current answers into polar coordinates, we can express the values in $Re^{\pm j\theta}$ format as well as R, θ format.
- The $Re^{\pm j\theta}$ is very important in the inverse transforms.

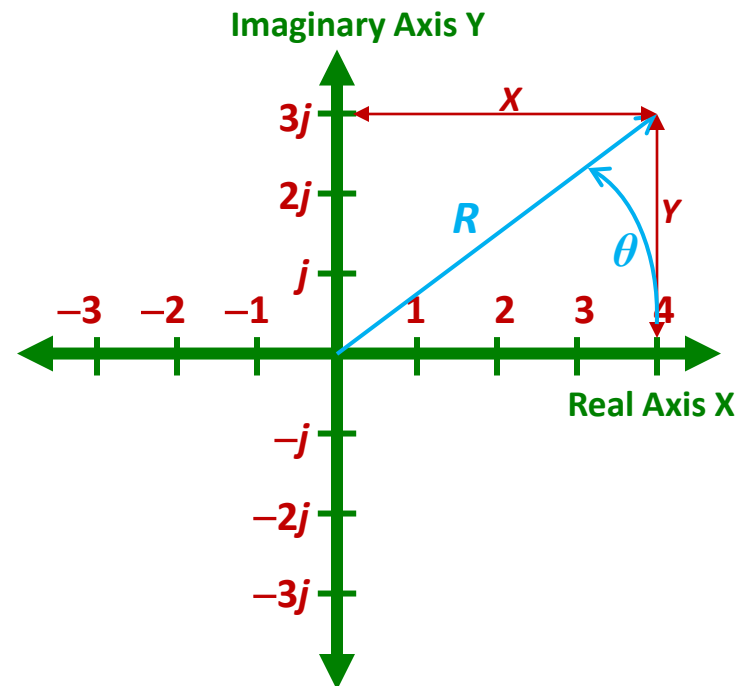

Inverse Transform Methodology

- We seek a time-domain current solution of the form $i(t) = I_p \cos(\omega t)$. where I_p is some peak current.
- This is difficult to do with the ω -domain answer in Cartesian ($A \pm jB$) form.
- So, we convert the ω -domain current solution to R, θ format, then convert that form to the $Re^{\pm j\theta}$ form, where we know that $\theta = \arctan(Y/X)$, and $R = \sqrt{X^2 + Y^2}$.
- Once the ω -domain current is in $Re^{\pm j\theta}$ form (and skipping a lot of derivation), we can get the time-domain current as follows:

Inverse Transform Methodology (2)


- **Given the $Re^{\pm j\theta}$ expression of the ω -domain current, we have only to do two things:**
 - Multiply the $Re^{\pm j\theta}$ expression by $e^{j\omega t}$.
 - Take the real part.
- **This may seem a little magical at this point, but remember, $\text{Re}(e^{j\omega t})$ is $\cos \omega t$, and we are looking for a current that is a cosine function of time.**
- **We can see examples of this methodology by converting our four ω -domain current solutions to real time-domain answers.**

Transforming Solutions

- In the resistor case, our ω -domain current is a real number, 0.1 A. Then $X=0.1$, $Y=0$.
- Then $R = \sqrt{X^2 + Y^2} = \sqrt{(0.1)^2} = 0.1$, and $\theta = \arctan Y/X = \arctan 0 = 0$.
- Thus current = $\text{Re} \{0.1 e^{j\omega t} e^{j0}\} = 0.1 \text{Re} \{0.1 e^{j\omega t}\} = 0.1 \cos 1000t$ A.
- Physically, this means that the AC current is cosinusoidal, like the voltage. It rises and falls in lock step with the voltages, and has a maximum value of 0.1 A (figure at right).


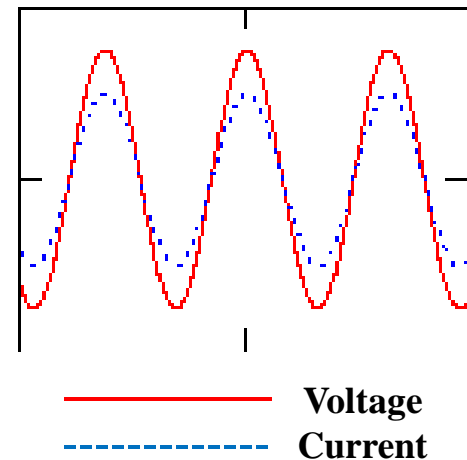
$$\omega\text{-domain current} = V_p / R \\ = 10/100 = 0.1 \text{ ampere}$$




Transforming Solutions (2)

- For the inductor circuit, $I = -j1 = -j$.
- Converting to polar: $R = \sqrt{X^2 + Y^2} = \sqrt{(1)^2} = 1$
- $\theta = \arctan Y/X = \arctan -1/0 = \arctan -\infty = -90^\circ$.
- $I_\omega = 1, -90^\circ = 1e^{-j90^\circ} = e^{-j90^\circ}$.
- Multiplying by $e^{j\omega t}$ and taking the real part: $i(t) = \text{Re}\{e^{j\omega t} \cdot e^{-j90^\circ}\} = \text{Re}\{e^{j(\omega t - 90^\circ)}\} = (1)\cos(\omega t - 90^\circ) = \cos(\omega t - 90^\circ)$ A.
- Physical interpretation: $i(t)$ is a maximum of 1 A, is cosinusoidal like the voltage, but lags the voltage by exactly 90° (plot at right).
- The angle θ between voltage and current is called the phase angle. $\cos \theta$ is called the power factor, a measure of power dissipation in an inductor or capacitor circuit.



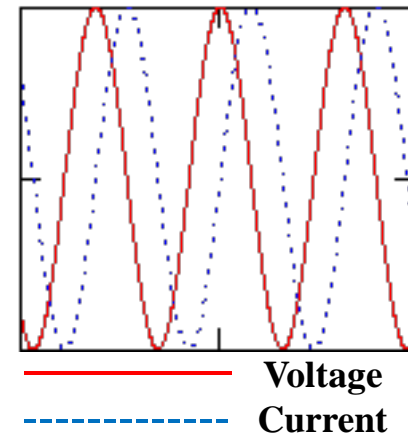
ω -domain current = $V_p / j\omega L$
 $= 10/j10 = -j1 = -j$ ampere




Transforming Solutions (3)

- For the capacitor circuit, $I = -j$ A.
- Converting to polar:

$$R = \sqrt{X^2 + Y^2} = \sqrt{(-1)^2} = 1 \quad .$$
- $\theta = \arctan Y/X = \arctan 1/0 = \arctan \infty = 90^\circ$, so that $I_\omega = 1, 90^\circ = e^{j90^\circ}$.
- Multiplying by $e^{j\omega t}$ and taking the real part: $i(t) = \text{Re}\{e^{j\omega t} \cdot e^{j90^\circ}\} = \text{Re}\{e^{j(\omega t + 90^\circ)}\} = \cos(\omega t + 90^\circ)$ A.
- Physically, $i(t)$ has a maximum amplitude of 1 A, is cosinusoidal like the voltage, but leads the voltage by exactly 90° (figure at right).

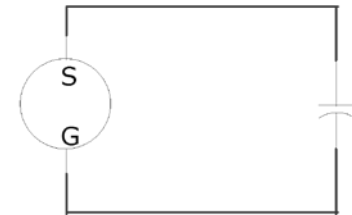
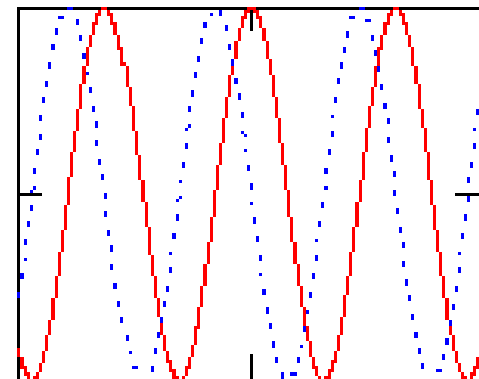
$$\begin{aligned} \omega\text{-domain current} &= V_p / (1/j\omega C) \\ &= 1 / -j0.1 = j10 \text{ amperes} \end{aligned}$$




— Voltage
 - - - Current

Transforming Solutions (4)

- For the RL circuit, $I = 0.5 - j0.5$ ampere.
- Converting to polar:

$$R = \sqrt{X^2 + Y^2} = \sqrt{(0.5)^2 + (-0.5)^2} \approx 0.707.$$
- And $\theta = \arctan Y/X = \arctan -0.5/0.5 = \arctan -1 = -45^\circ$; $I_\omega = 0.707, -90^\circ = 0.707e^{-j45^\circ}$.
- Multiplying by $e^{j\omega t}$ and taking the real part:

$$i(t) = \text{Re}\{0.707e^{j\omega t} \cdot e^{-j45^\circ}\} = 0.707\text{Re}\{e^{j(\omega t - 45^\circ)}\} = 0.707\cos(\omega t - 45^\circ) = 0.707\cos(\omega t - 45^\circ) \text{ A}.$$
- Note the physical interpretation: $i(t)$ has a maximum amplitude of 0.707 A, is cosinusoidal like the voltage, and lags the voltage by 45°. Lagging current is an inductive characteristic, but it is less than 90°, due to the influence of the resistor.

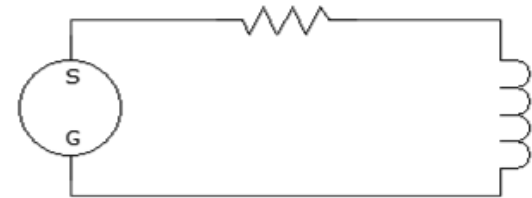

$$\begin{aligned} \omega\text{-domain current} &= V_p / (R + j\omega L) \\ &= 10 / (10 + j10) = 0.5 - j0.5 \text{ ampere} \end{aligned}$$

Summary: Solving for Currents Using ω Transforms

- Transform values to the ω -domain:

Element	Time Domain	ω Domain Transform
AC Voltage	$V_p \cos \omega t$	V_p
Resistance	R	R
Inductance	L	$j\omega L$
Capacitance	C	$1/j\omega C$

- Solve for I_ω , using Ohm's and Kirchoff's laws.
 - Solution will be of the form $A \pm jB$ (Cartesian complex plane).
- Use inverse transforms to obtain $i(t)$.
 - Convert the Cartesian solution ($A \pm jB$) to R, θ format and thence to $Re^{\pm j\theta}$ form.
 - Multiply by $e^{\pm j\omega t}$ and take the real part to get a cosine-expression for $i(t)$.

Measuring AC Current Indirectly

- Because we do not have current probes for the oscilloscope, we will use an indirect measurement to find $i(t)$ (reference Figs. 11 and 13 in Exercise 5).
- As the circuit resistance is real, it does not contribute to the phase angle of the current. Then a measure of voltage across the circuit resistance is a direct measure of the phase of $i(t)$.
- Further, a measure of the Δt between the i, v peaks is a direct measure of the phase difference in seconds.
- We will use this method to determine the actual phase angle and magnitude of the current in Lab. 5.



Discovery Exercises

- Lab. 5 includes two exercises that uses inductive and capacitive impedance calculations to allow the discovery of the equivalent inductance of series inductors and the equivalent capacitance of series capacitors.
- Question 7.6 then asks you to infer the equivalent inductance of parallel inductors and the equivalent capacitance of parallel capacitors.
- Although you are really making an educated guess at that point, you can validate your guess using ω -domain circuit theory, with one additional bit of knowledge not covered in the lab text:
 - In the ω -domain, parallel impedances add reciprocally, just like resistances in a DC circuit.
 - (Remember that in the ω -domain, series impedances add directly).