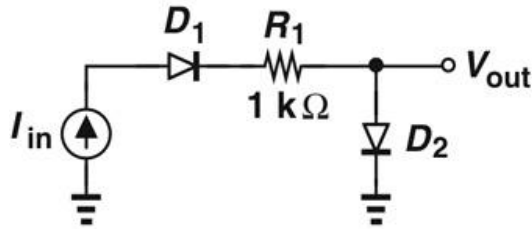


UNIVERSITY OF TEXAS AT DALLAS
Department of Electrical Engineering
EE/CE 3311 – Electronic Circuits
 Assignment II


Date assigned: 9/10/2012
 Date due: 9/17/2012

Problem 2.1

Beginning with $V_{D,on}=800$ mV for each diode, determine the change in V_{out} if I_{in} changes from 3mA to 3.1mA for the circuits shown below.



(a)

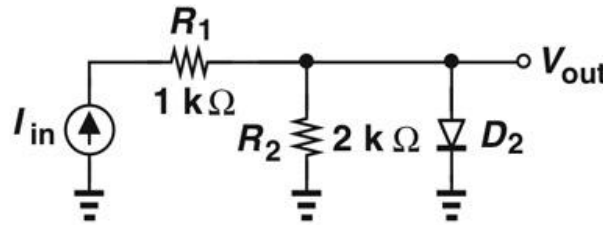


(b)


Problem 2.2

Plot the input/output characteristics of the circuits below. Assume a constant-voltage model. Assume $R_1=1K$ and $R_2=2K$ and $V_B=2V$.


(a)

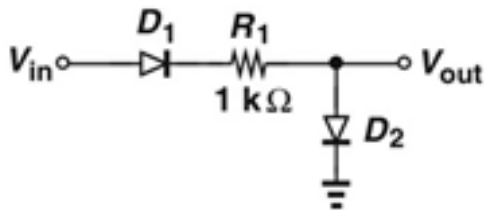


(b)

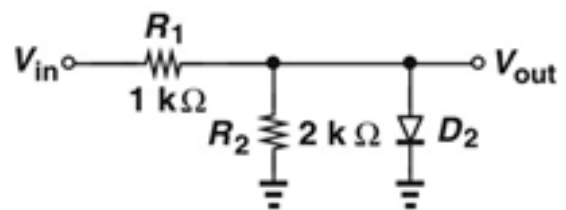

(c)

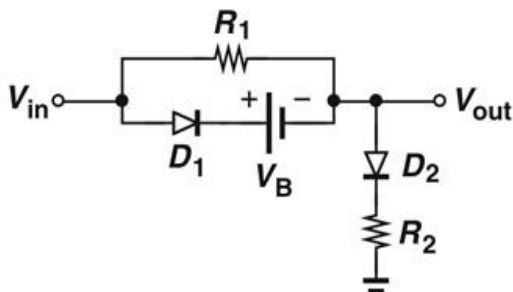


(d)

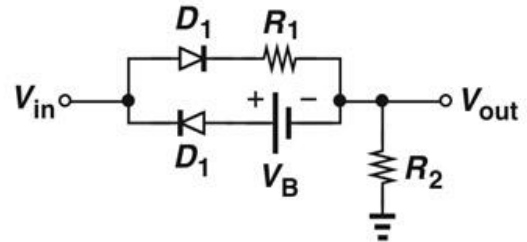

Problem 2.3

Assuming $V_{in} = V_p \sin wt$, plot the output waveform of the circuit shown below for an initial condition of 0.5V across C_1 . You can assume $V_p = 5V$.

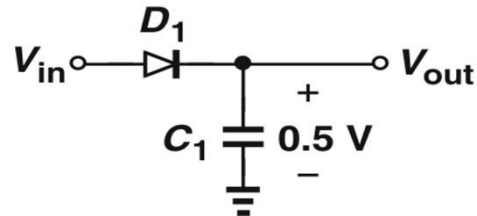

Problem 2.4 Pspice Simulation Assignment

Problem 3.52 in Fundamentals of Microelectronics by Razavi