

Fundamentals of Microelectronics

- CH1 Why Microelectronics?
- CH2 Basic Physics of Semiconductors
- CH3 Diode Circuits
- CH4 Physics of Bipolar Transistors
- CH5 Bipolar Amplifiers
- CH6 Physics of MOS Transistors
- CH7 CMOS Amplifiers
- CH8 Operational Amplifier As A Black Box

1

Chapter 5 Bipolar Amplifiers

- 5.1 General Considerations
- 5.2 Operating Point Analysis and Design
- 5.3 Bipolar Amplifier Topologies
- 5.4 Summary and Additional Examples

2

Bipolar Amplifiers

General Concepts

- Input and Output Impedances
- Biasing
- DC and Small-Signal Analysis


Operating Point Analysis

- Simple Biasing
- Emitter Degeneration
- Self-Biasing
- Biasing of PNP Devices

Amplifier Topologies


- Common-Emitter Stage
- Common-Base Stage
- Emitter Follower

Voltage Amplifier

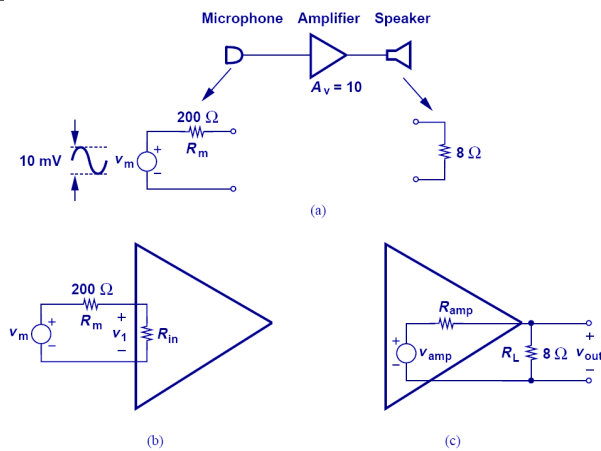


- In an ideal voltage amplifier, the input impedance is infinite and the output impedance zero.
- But in reality, input or output impedances depart from their ideal values.

Input/Output Impedances

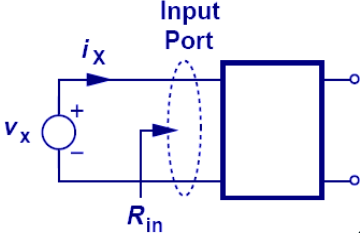

(a)

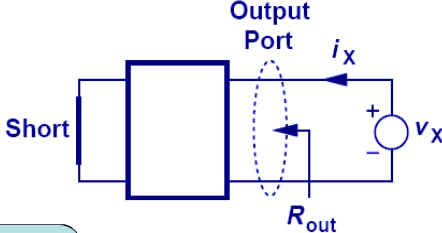


(b)

$$R_x = \frac{V_x}{i_x}$$


➤ The figure above shows the techniques of measuring input and output impedances.

CH5 Bipolar Amplifiers 5

Input Impedance Example I

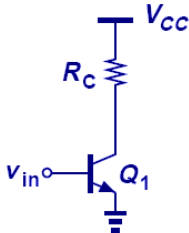

(a)

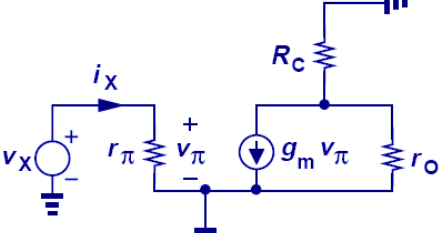


(b)

$$\frac{v_x}{i_x} = r_\pi$$

➤ When calculating input/output impedance, small-signal analysis is assumed.

CH5 Bipolar Amplifiers 6

Impedance at a Node

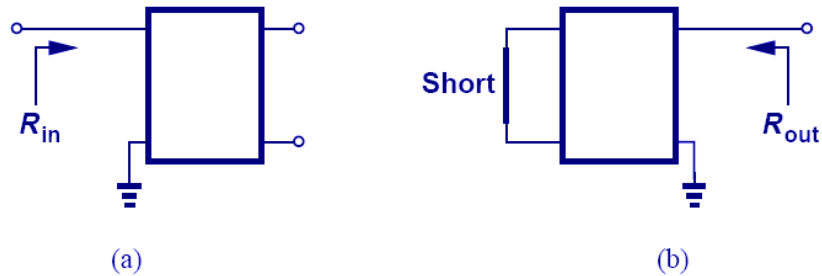


- When calculating I/O impedances at a port, we usually ground one terminal while applying the test source to the other terminal of interest.

CH5 Bipolar Amplifiers

7

Impedance at Collector

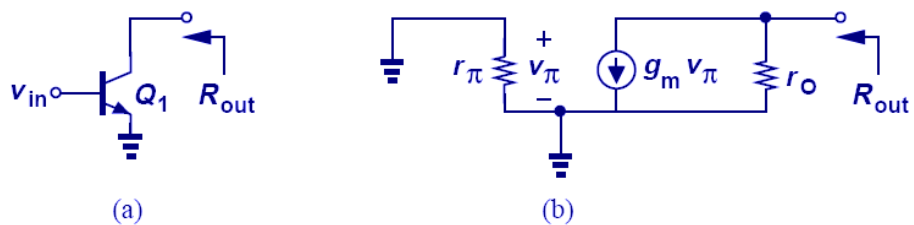


$$R_{out} = r_o$$

- With Early effect, the impedance seen at the collector is equal to the intrinsic output impedance of the transistor (if emitter is grounded).


CH5 Bipolar Amplifiers

8

Impedance at Emitter

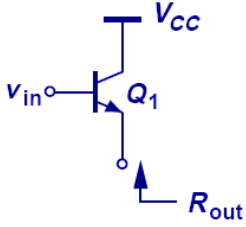

(a)

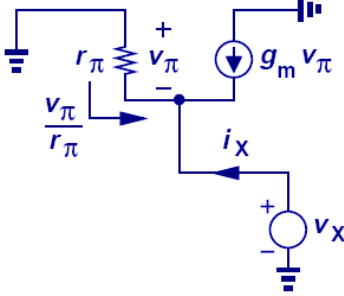

(b)

$$\frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{r_\pi}}$$


$$R_{out} \approx \frac{1}{g_m}$$

$(V_A = \infty)$


➤ The impedance seen at the emitter of a transistor is approximately equal to one over its transconductance (if the base is grounded).

CH5 Bipolar Amplifiers
9

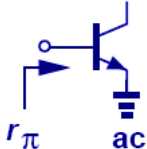
Three Master Rules of Transistor Impedances



r_π ac

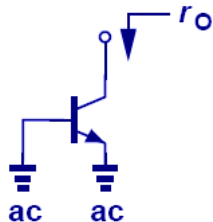

r_o ac ac

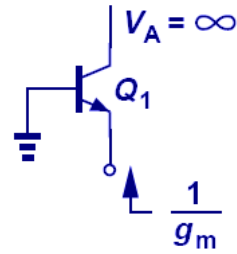

$V_A = \infty$
 Q_1
 $\frac{1}{g_m}$

➤ Rule # 1: looking into the base, the impedance is r_π if emitter is (ac) grounded.

➤ Rule # 2: looking into the collector, the impedance is r_o if emitter is (ac) grounded.

➤ Rule # 3: looking into the emitter, the impedance is $1/g_m$ if base is (ac) grounded and Early effect is neglected.

CH5 Bipolar Amplifiers
10

Biasing of BJT

V_{BE} Bias (dc) Value

I_C Bias (dc) Value

➤ **Transistors and circuits must be biased because (1) transistors must operate in the active region, (2) their small-signal parameters depend on the bias conditions.**

CH5 Bipolar Amplifiers 11

DC Analysis vs. Small-Signal Analysis

DC Analysis

⇒

≡ Short
 ≡ Open


Small-Signal Analysis

➤ **First, DC analysis is performed to determine operating point and obtain small-signal parameters.**

➤ **Second, sources are set to zero and small-signal model is used.**

CH5 Bipolar Amplifiers 12

Notation Simplification

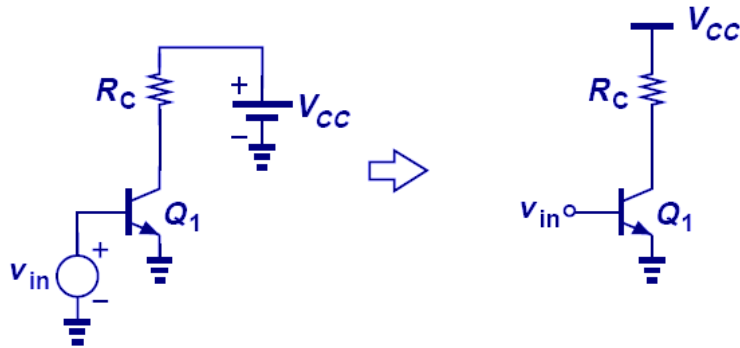


- Hereafter, the battery that supplies power to the circuit is replaced by a horizontal bar labeled V_{CC} , and input signal is simplified as one node called V_{in} .

CH5 Bipolar Amplifiers

13

Example of Bad Biasing

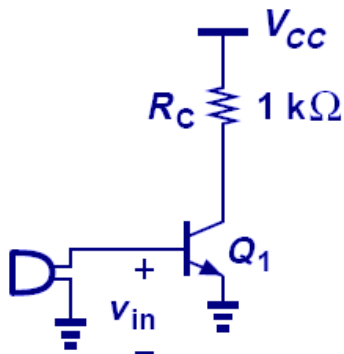


- The microphone is connected to the amplifier in an attempt to amplify the small output signal of the microphone.
- Unfortunately, there's no DC bias current running thru the transistor to set the transconductance.

CH5 Bipolar Amplifiers

14

Another Example of Bad Biasing

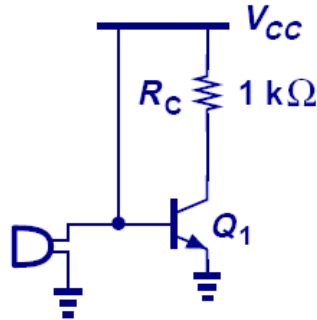


- The base of the amplifier is connected to V_{CC}, trying to establish a DC bias.
- Unfortunately, the output signal produced by the microphone is shorted to the power supply.

CH5 Bipolar Amplifiers

15

Biasing with Base Resistor

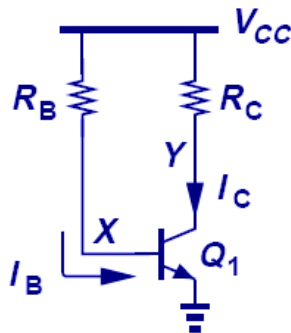


$$I_B = \frac{V_{CC} - V_{BE}}{R_B}, I_C = \beta \frac{V_{CC} - V_{BE}}{R_B}$$

- Assuming a constant value for V_{BE}, one can solve for both I_B and I_C and determine the terminal voltages of the transistor.
- However, bias point is sensitive to β variations.

CH5 Bipolar Amplifiers

16

Improved Biasing: Resistive Divider

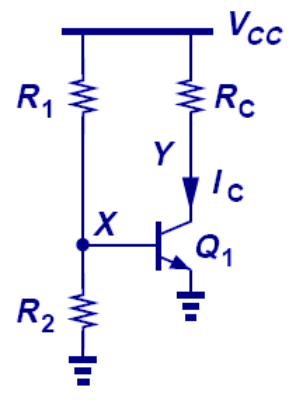


$$V_X = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$I_C = I_S \exp\left(\frac{R_2}{R_1 + R_2} \frac{V_{CC}}{V_T}\right)$$

➤ Using resistor divider to set V_{BE} , it is possible to produce an I_C that is relatively independent of β if base current is small.


Accounting for Base Current

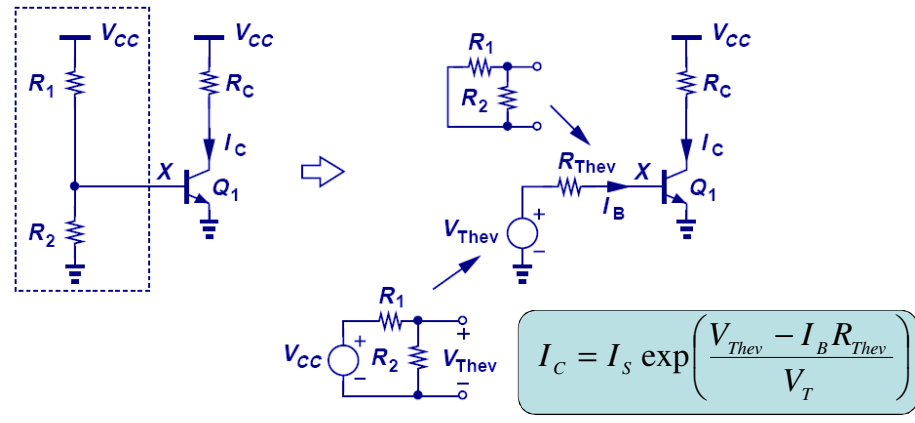

$$I_C = I_S \exp\left(\frac{V_{Thev} - I_B R_{Thev}}{V_T}\right)$$

➤ With proper ratio of R_1 and R_2 , I_C can be insensitive to β ; however, its exponential dependence on resistor deviations makes it less useful.

Emitter Degeneration Biasing

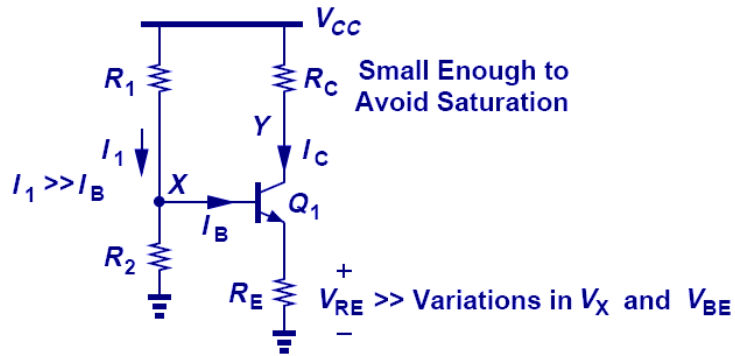

- The presence of R_E helps to absorb the error in V_X so V_{BE} stays relatively constant.
- This bias technique is less sensitive to β ($I_1 \gg I_B$) and V_{BE} variations.

CH5 Bipolar Amplifiers


19

Design Procedure

- Choose an I_C to provide the necessary small signal parameters, g_m , r_{π} , etc.
- Considering the variations of R_1 , R_2 , and V_{BE} , choose a value for V_{RE} .
- With V_{RE} chosen, and V_{BE} calculated, V_X can be determined.
- Select R_1 and R_2 to provide V_X .

20

Self-Biasing Technique

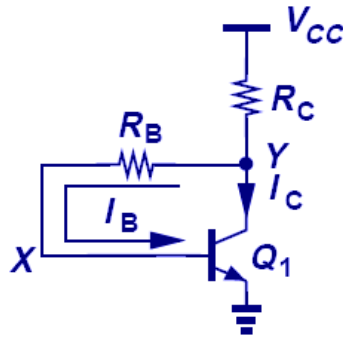

- This bias technique utilizes the collector voltage to provide the necessary V_x and I_B .
- One important characteristic of this technique is that collector has a higher potential than the base, thus guaranteeing active operation of the transistor.

CH5 Bipolar Amplifiers

21

Self-Biasing Design Guidelines

$$(1) \quad R_C \gg \frac{R_B}{\beta}$$

$$(2) \quad \Delta V_{BE} \ll V_{CC} - V_{BE}$$

- (1) provides insensitivity to β .
- (2) provides insensitivity to variation in V_{BE} .

CH5 Bipolar Amplifiers

22

Summary of Biasing Techniques

V_{CC}
 R_B R_C Q_1
 Sensitive to β

V_{CC}
 R_1 R_2 R_C Q_1
 Sensitive to Resistor Error

V_{CC}
 R_1 R_2 R_C R_E Q_1
 I_1 V_{RE}
 Always in Active Mode

CH5 Bipolar Amplifiers 23

PNP Biasing Techniques

V_{CC}
 R_B R_C Q_1
 I_B V_{EB}^+ V_{EB}^- I_C

V_{CC}
 R_2 R_1 R_C Q_1
 I_1 I_B V_{EB}^+ V_{EB}^- I_C


V_{CC}
 R_2 R_1 R_C R_E Q_1
 I_1 I_B V_{EB}^+ V_{EB}^- V_{RE}^- I_C

V_{CC}
 R_2 R_1 R_C R_E Q_1
 I_1 I_B V_{EB}^+ V_{EB}^- V_{RE}^- I_C

➤ Same principles that apply to NPN biasing also apply to PNP biasing with only polarity modifications.

CH5 Bipolar Amplifiers 24

Possible Bipolar Amplifier Topologies

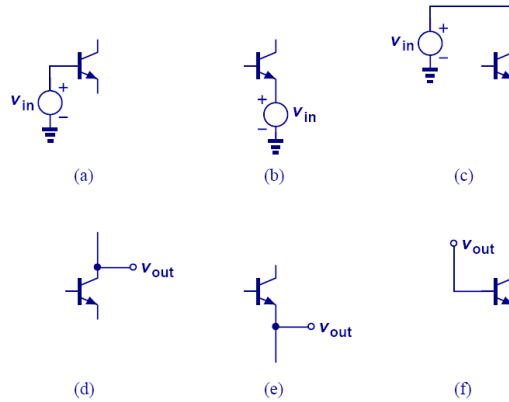

- Three possible ways to apply an input to an amplifier and three possible ways to sense its output.
- However, in reality only three of six input/output combinations are useful.

CH5 Bipolar Amplifiers

25

Study of Common-Emitter Topology

- *Analysis of CE Core*
Inclusion of Early Effect
- *Emitter Degeneration*
Inclusion of Early Effect
- *CE Stage with Biasing*

26

Common-Emitter Topology

Input Applied to Base

Output Sensed at Collector

CH5 Bipolar Amplifiers 27

Small Signal of CE Amplifier

$$A_v = \frac{v_{out}}{v_{in}}$$


$$-\frac{v_{out}}{R_C} = g_m v_\pi = g_m v_{in}$$

$$A_v = -g_m R_C$$

Current

CH5 Bipolar Amplifiers 28



Limitation on CE Voltage Gain

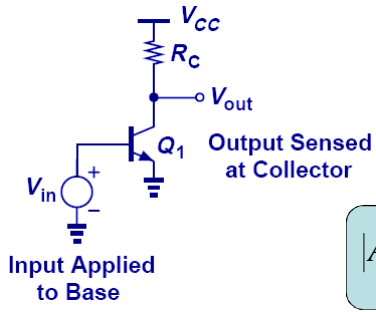


$$|A_v| = \frac{I_C R_C}{V_T} \quad |A_v| = \frac{V_{RC}}{V_T} \quad |A_v| < \frac{V_{CC} - V_{BE}}{V_T}$$

- Since g_m can be written as I_C/V_T , the CE voltage gain can be written as the ratio of V_{RC} and V_T .
- V_{RC} is the potential difference between V_{CC} and V_{CE} , and V_{CE} cannot go below V_{BE} in order for the transistor to be in active region.

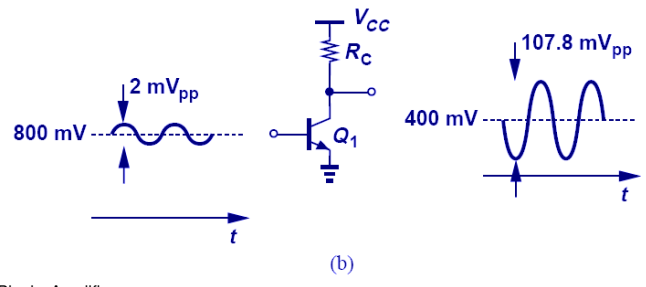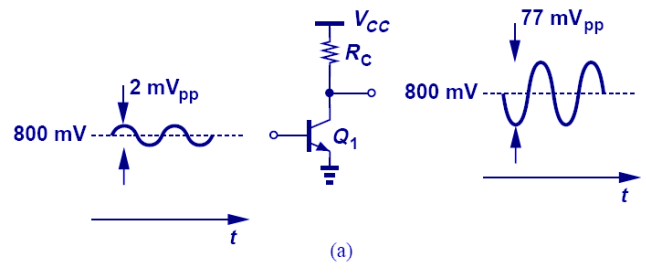
Tradeoff between Voltage Gain and Headroom



I/O Impedances of CE Stage

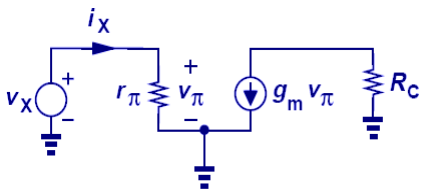

(a)

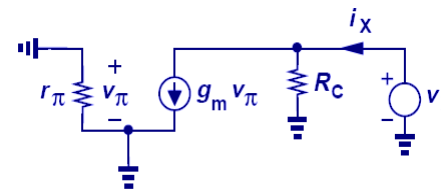

(b)

$$R_{in} = \frac{v_X}{i_X} = r_{\pi}$$

$$R_{out} = \frac{v_X}{i_X} = R_C$$

➤ When measuring output impedance, the input port has to be grounded so that $V_{in} = 0$.

CH5 Bipolar Amplifiers
31

CE Stage Trade-offs

Voltage Headroom (Swings)

↕

Voltage Gain

↙

g_m

Input Impedance

$\frac{\beta}{g_m}$

↘


R_C

Output Impedance

R_C

CH5 Bipolar Amplifiers
32

Inclusion of Early Effect

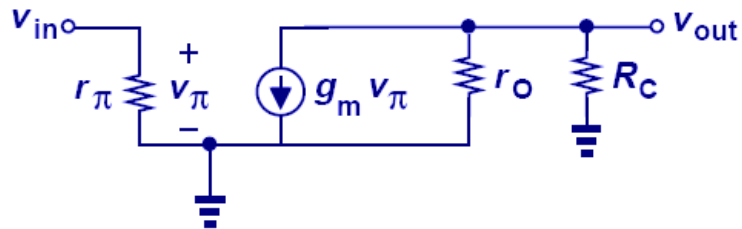

$$A_v = -g_m (R_C \parallel r_o)$$

$$R_{out} = R_C \parallel r_o$$

- Early effect will lower the gain of the CE amplifier, as it appears in parallel with R_C .

CH5 Bipolar Amplifiers

33

Intrinsic Gain

$$A_v = -g_m r_o$$

$$|A_v| = \frac{V_A}{V_T}$$

- As R_C goes to infinity, the voltage gain reaches the product of g_m and r_o , which represents the maximum voltage gain the amplifier can have.
- The intrinsic gain is independent of the bias current.

CH5 Bipolar Amplifiers

34

Current Gain

$$A_I = \frac{i_{out}}{i_{in}}$$


$$A_I|_{CE} = \beta$$

- Another parameter of the amplifier is the current gain, which is defined as the ratio of current delivered to the load to the current flowing into the input.
- For a CE stage, it is equal to β .


CH5 Bipolar Amplifiers

35

Emitter Degeneration

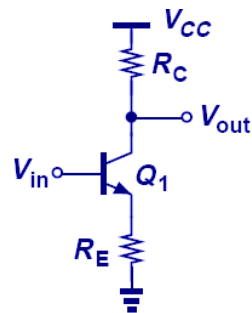

(a)

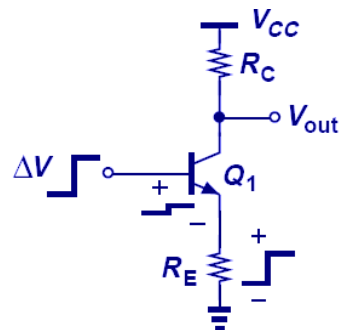


(b)

- By inserting a resistor in series with the emitter, we “degenerate” the CE stage.
- This topology will decrease the gain of the amplifier but improve other aspects, such as linearity, and input impedance.

CH5 Bipolar Amplifiers

36

Small-Signal Model

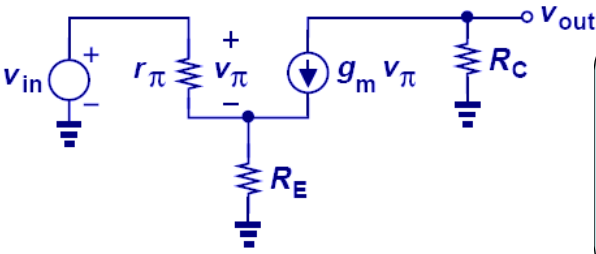



$$A_v = -\frac{g_m R_C}{1 + g_m R_E}$$

$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$

➤ Interestingly, this gain is equal to the total load resistance to ground divided by $1/g_m$ plus the total resistance placed in series with the emitter.

CH5 Bipolar Amplifiers
37

Emitter Degeneration Example I

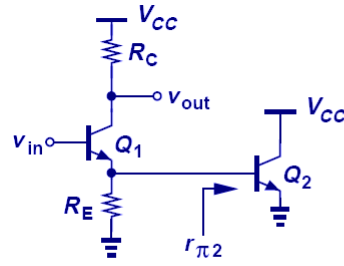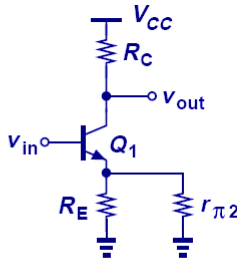



$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + R_E \parallel r_{\pi 2}}$$

➤ The input impedance of Q_2 can be combined in parallel with R_E to yield an equivalent impedance that degenerates Q_1 .

CH5 Bipolar Amplifiers
38


Emitter Degeneration Example II

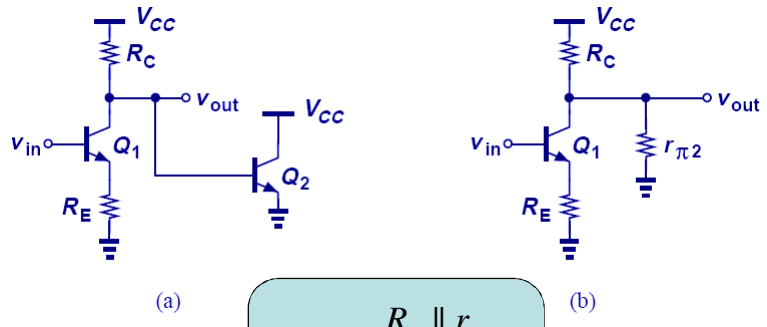

$$A_v = - \frac{R_C \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

➤ In this example, the input impedance of Q_2 can be combined in parallel with R_C to yield an equivalent collector impedance to ground.

Input Impedance of Degenerated CE Stage

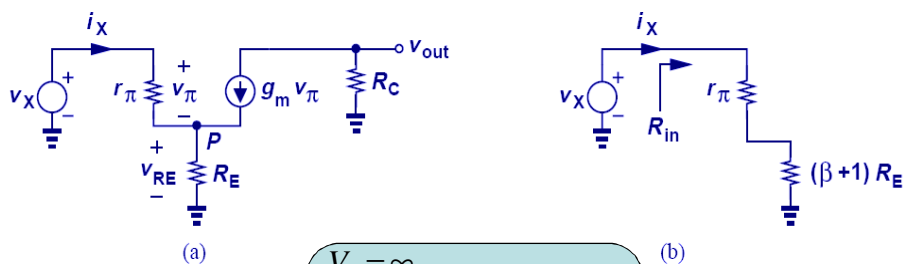


$$V_A = \infty$$

$$v_X = r_{\pi} i_X + R_E (1 + \beta) i_X$$

$$R_{in} = \frac{v_X}{i_X} = r_{\pi} + (\beta + 1) R_E$$

➤ With emitter degeneration, the input impedance is increased from r_{π} to $r_{\pi} + (\beta + 1) R_E$; a desirable effect.

Output Impedance of Degenerated CE Stage

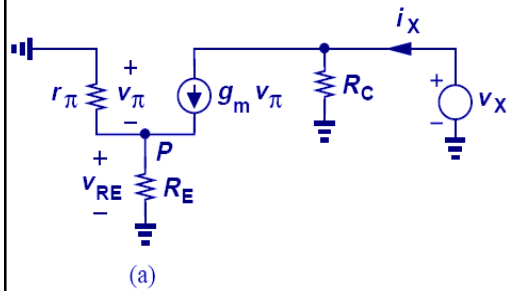

$$V_A = \infty$$

$$v_{in} = 0 = v_{\pi} + \left(\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) R_E \Rightarrow v_{\pi} = 0$$


$$R_{out} = \frac{v_x}{i_x} = R_C$$

- Emitter degeneration does not alter the output impedance in this case. (More on this later.)

CH5 Bipolar Amplifiers

41

Capacitor at Emitter

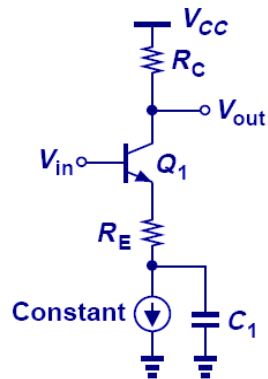


- At DC the capacitor is open and the current source biases the amplifier.
- For ac signals, the capacitor is short and the amplifier is degenerated by R_E .


CH5 Bipolar Amplifiers

42

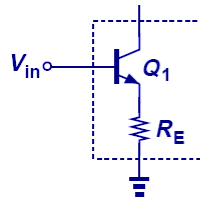Example: Design CE Stage with Degeneration as a Black Box



(a)

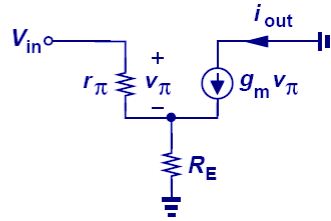

(b)



$$V_A = \infty$$

$$i_{out} = g_m \frac{v_{in}}{1 + (r_{\pi}^{-1} + g_m)R_E}$$

$$G_m = \frac{i_{out}}{v_{in}} \approx \frac{g_m}{1 + g_m R_E}$$

➤ If $g_m R_E$ is much greater than unity, G_m is more linear.

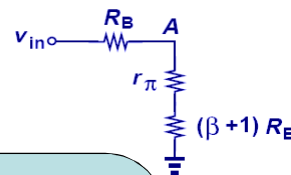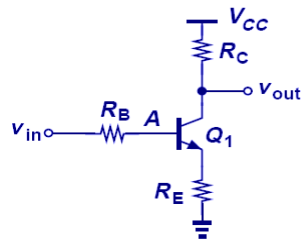Degenerated CE Stage with Base Resistance




$$V_A = \infty$$

$$\frac{v_{out}}{v_{in}} = \frac{v_A}{v_{in}} \cdot \frac{v_{out}}{v_A}$$

$$\frac{v_{out}}{v_{in}} = \frac{-\beta R_C}{r_{\pi} + (\beta + 1)R_E + R_B}$$

$$A_v \approx \frac{-R_C}{\frac{1}{g_m} + R_E + \frac{R_B}{\beta + 1}}$$

Input/Output Impedances

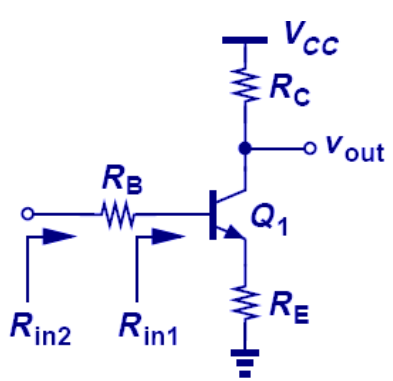

$V_A = \infty$

$R_{in1} = r_{\pi} + (\beta + 1)R_E$



$R_{in2} = R_B + r_{\pi2} + (\beta + 1)R_E$

$R_{out} = R_C$

➤ R_{in1} is more important in practice as R_B is often the output impedance of the previous stage.

CH5 Bipolar Amplifiers
45

Emitter Degeneration Example III

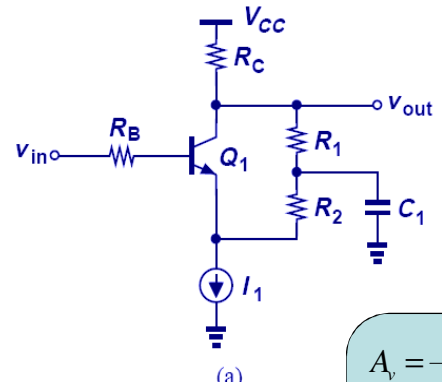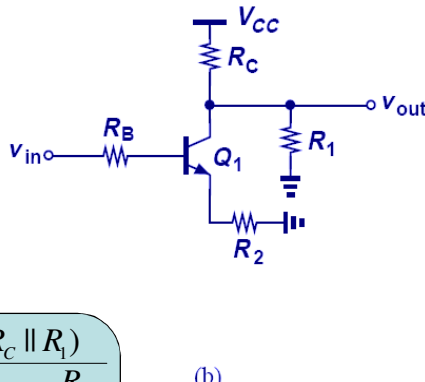
$A_v = \frac{-(R_C \parallel R_1)}{\frac{1}{g_m} + R_2 + \frac{R_B}{\beta + 1}}$

$R_{in} = r_{\pi} + (\beta + 1)R_2$


$R_{out} = R_C \parallel R_1$

CH5 Bipolar Amplifiers
46

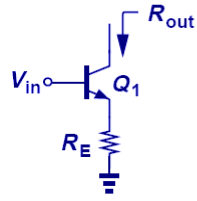Output Impedance of Degenerated Stage with $V_A < \infty$



(a)

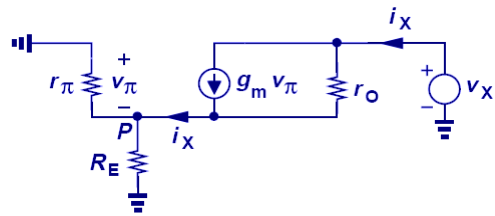

(b)


$$R_{out} = [1 + g_m (R_E \parallel r_\pi)] r_o + R_E \parallel r_\pi$$

$$R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$

$$R_{out} \approx r_o [1 + g_m (R_E \parallel r_\pi)]$$


- Emitter degeneration boosts the output impedance by a factor of $1 + g_m(R_E \parallel r_\pi)$.
- This improves the gain of the amplifier and makes the circuit a better current source.

Two Special Cases

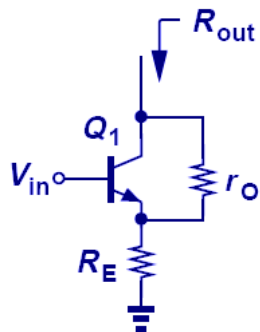

- 1) $R_E \gg r_\pi$
 $R_{out} \approx r_o (1 + g_m r_\pi) \approx \beta r_o$
- 2) $R_E \ll r_\pi$
 $R_{out} \approx (1 + g_m R_E) r_o$

Analysis by Inspection

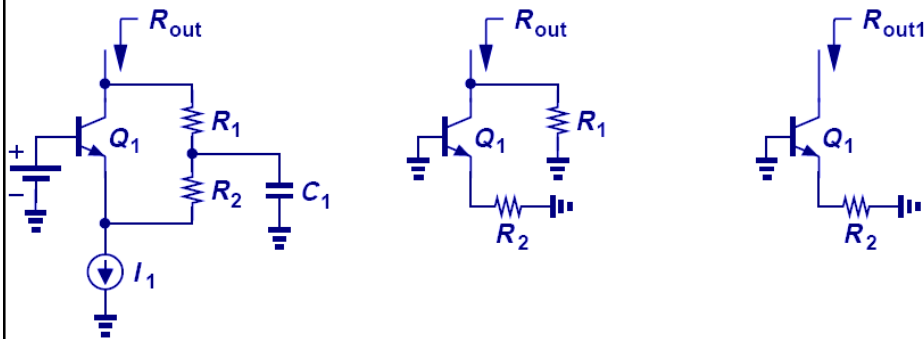


$$R_{out} = R_1 \parallel R_{out1} \implies R_{out1} = [1 + g_m (R_2 \parallel r_\pi)] r_o \implies R_{out} = [1 + g_m (R_2 \parallel r_\pi)] r_o \parallel R_1$$

➤ This seemingly complicated circuit can be greatly simplified by first recognizing that the capacitor creates an AC short to ground, and gradually transforming the circuit to a known topology.

CH5 Bipolar Amplifiers
49

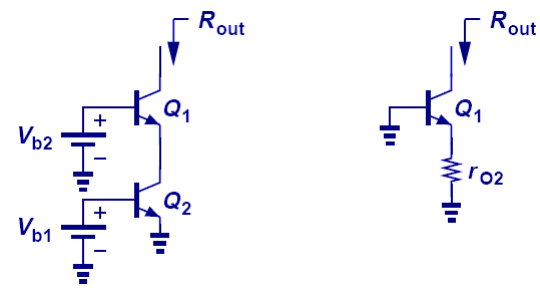Example: Degeneration by Another Transistor



$$R_{out} = [1 + g_{m1} (r_{O2} \parallel r_{\pi1})] r_{O1}$$

➤ Called a “cascode”, the circuit offers many advantages that are described later in the book.


CH5 Bipolar Amplifiers
50

Study of Common-Emitter Topology

- Analysis of CE Core
 - Inclusion of Early Effect
- Emitter Degeneration
 - Inclusion of Early Effect
- *CE Stage with Biasing*

51

Bad Input Connection

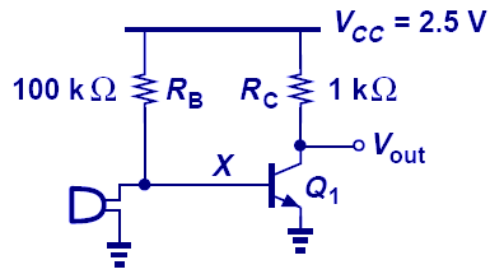


- Since the microphone has a very low resistance that connects from the base of Q_1 to ground, it attenuates the base voltage and renders Q_1 without a bias current.

CH5 Bipolar Amplifiers


52

Use of Coupling Capacitor

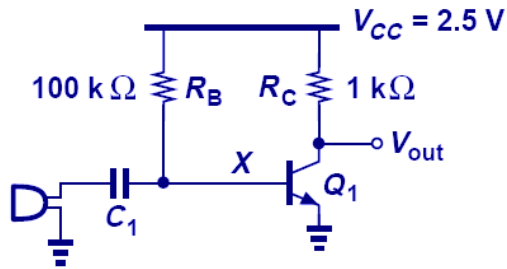

➤ Capacitor isolates the bias network from the microphone at DC but shorts the microphone to the amplifier at higher frequencies.

DC and AC Analysis

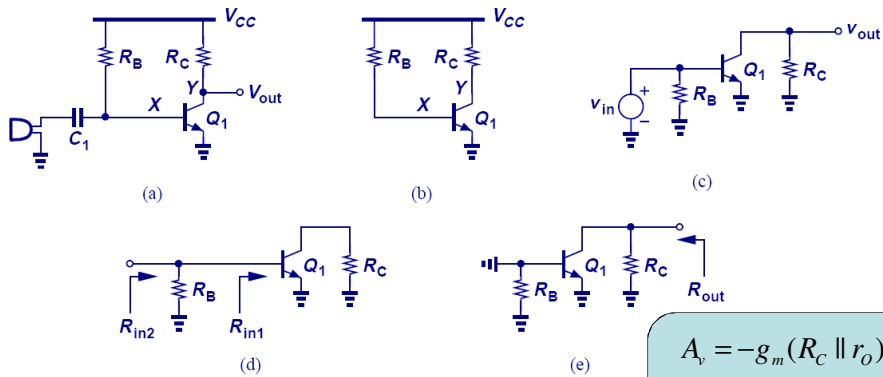


$$A_v = -g_m (R_C \parallel r_o)$$

$$R_{in} = r_\pi \parallel R_B$$

$$R_{out} = R_C \parallel r_o$$

➤ Coupling capacitor is open for DC calculations and shorted for AC calculations.

Bad Output Connection

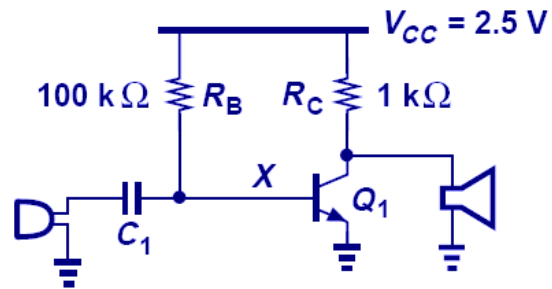


- Since the speaker has an inductor, connecting it directly to the amplifier would short the collector at DC and therefore push the transistor into deep saturation.

CH5 Bipolar Amplifiers

55

Still No Gain!!!

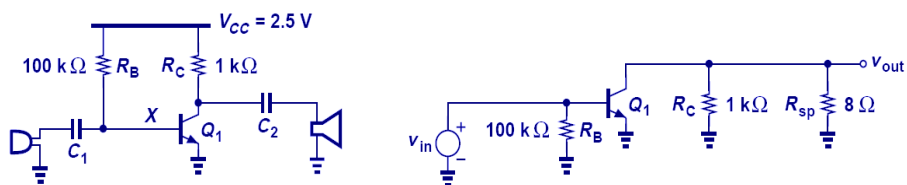


- In this example, the AC coupling indeed allows correct biasing. However, due to the speaker's small input impedance, the overall gain drops considerably.

CH5 Bipolar Amplifiers

56

CE Stage with Biasing

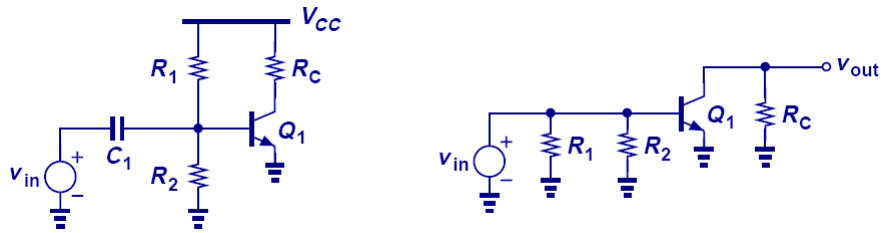

$$A_v = -g_m (R_C \parallel r_o)$$


$$R_{in} = r_\pi \parallel R_1 \parallel R_2$$

$$R_{out} = R_C \parallel r_o$$

CH5 Bipolar Amplifiers

57

CE Stage with Robust Biasing

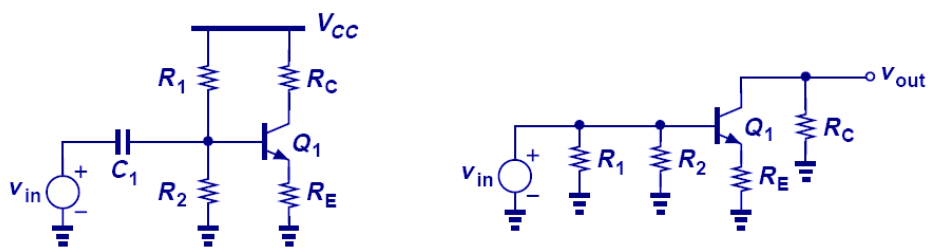

$$A_v = \frac{-R_C}{\frac{1}{g_m} + R_E}$$


$$R_{in} = [r_\pi + (\beta + 1)R_E] \parallel R_1 \parallel R_2$$

$$R_{out} = R_C$$

CH5 Bipolar Amplifiers

58

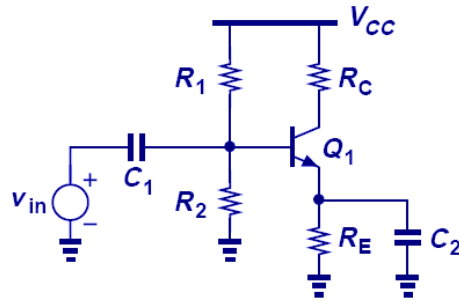Removal of Degeneration for Signals at AC




$$A_v = -g_m R_C$$

$$R_{in} = r_\pi \parallel R_1 \parallel R_2$$

$$R_{out} = R_C$$

➤ Capacitor shorts out R_E at higher frequencies and removes degeneration.

Complete CE Stage

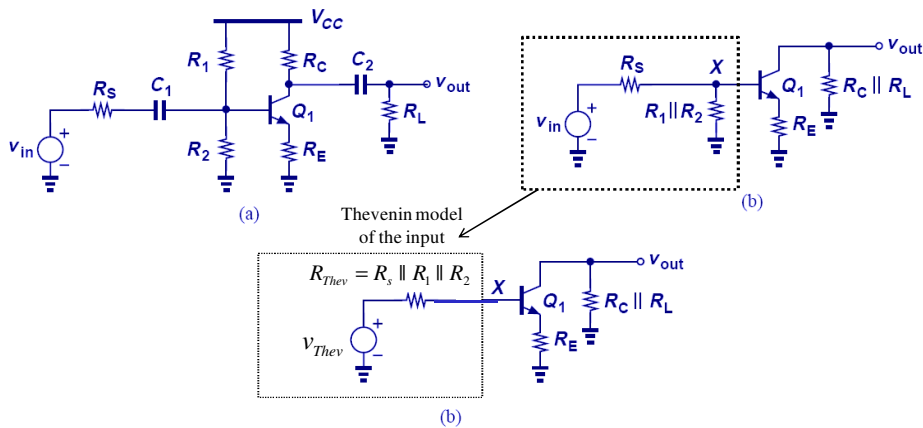

$$A_v = \frac{-R_C \parallel R_L}{\frac{1}{g_m} + R_E + \frac{R_s \parallel R_1 \parallel R_2}{\beta + 1}} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s}$$

$\frac{v_{out}}{v_{Thev}}$

Summary of CE Concepts

The summary includes the following key concepts and equations:

- Gain and Headroom:** $A_v = -g_m R_C$ and $A_v = -g_m (R_C \parallel r_o)$
- Input and Output Resistances:** R_{in} and R_{out}
- Emitter Resistor:** R_E
- Biasing Network:** $R_1, R_2, R_C, R_E, C_1, C_2$

CH5 Bipolar Amplifiers 61

Common Base (CB) Amplifier



Input Applied to Emitter

Output Sensed at Collector

➤ **In common base topology, where the base terminal is biased with a fixed voltage, emitter is fed with a signal, and collector is the output.**

CH5 Bipolar Amplifiers 62

CB Core

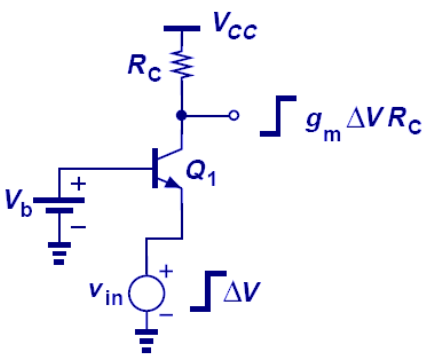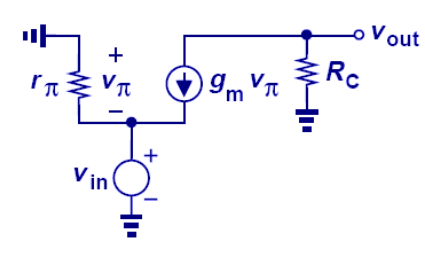



$$A_v = g_m R_C$$

➤ The voltage gain of CB stage is $g_m R_C$, which is identical to that of CE stage in magnitude and opposite in phase.

CH5 Bipolar Amplifiers
63

Tradeoff between Gain and Headroom

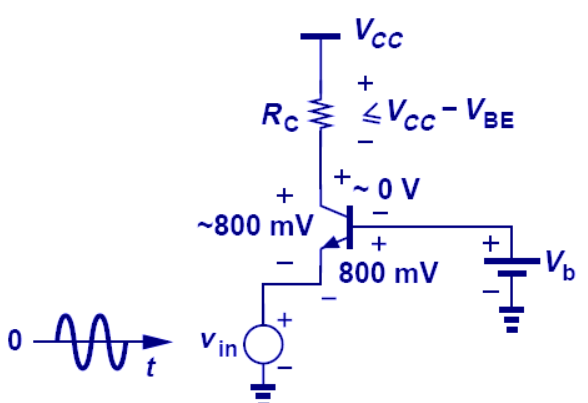

$$A_v = \frac{I_C}{V_T} \cdot R_C$$

$$= \frac{V_{CC} - V_{BE}}{V_T}$$

➤ To maintain the transistor out of saturation, the maximum voltage drop across R_C cannot exceed $V_{CC} - V_{BE}$.

CH5 Bipolar Amplifiers
64

Simple CB Example

Thermometer

$$A_v = g_m R_C = 17.2$$

$$R_1 = 22.3 \text{ K}\Omega$$

$$R_2 = 67.7 \text{ K}\Omega$$

CH5 Bipolar Amplifiers 65


Input Impedance of CB

$$R_{in} = \frac{1}{g_m}$$

➤ The input impedance of CB stage is much smaller than that of the CE stage.

CH5 Bipolar Amplifiers 66

Practical Application of CB Stage

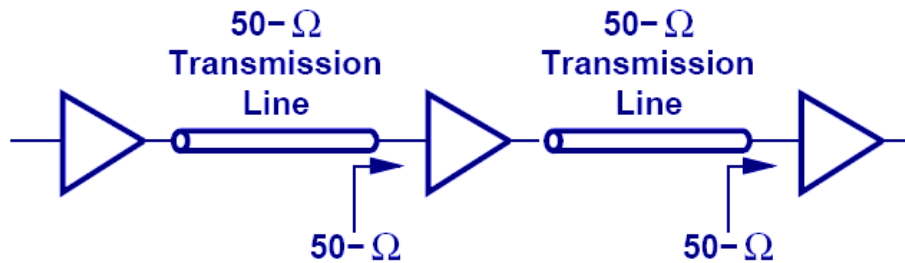


- To avoid “reflections”, need impedance matching.
- CB stage’s low input impedance can be used to create a match with 50 Ω .

CH5 Bipolar Amplifiers

67

Output Impedance of CB Stage

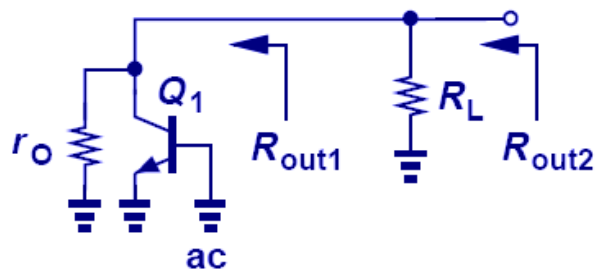


$$R_{out} = r_O \parallel R_C$$

- The output impedance of CB stage is similar to that of CE stage.

CH5 Bipolar Amplifiers


68

CB Stage with Source Resistance

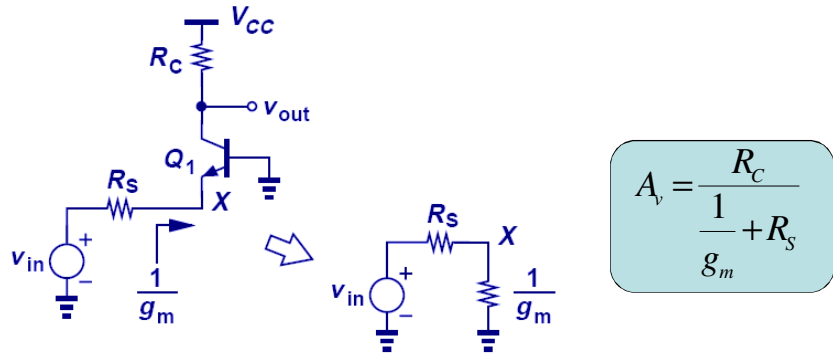

- With an inclusion of a source resistor, the input signal is attenuated before it reaches the emitter of the amplifier; therefore, we see a lower voltage gain.
- This is similar to CE stage emitter degeneration; only the phase is reversed.

Practical Example of CB Stage

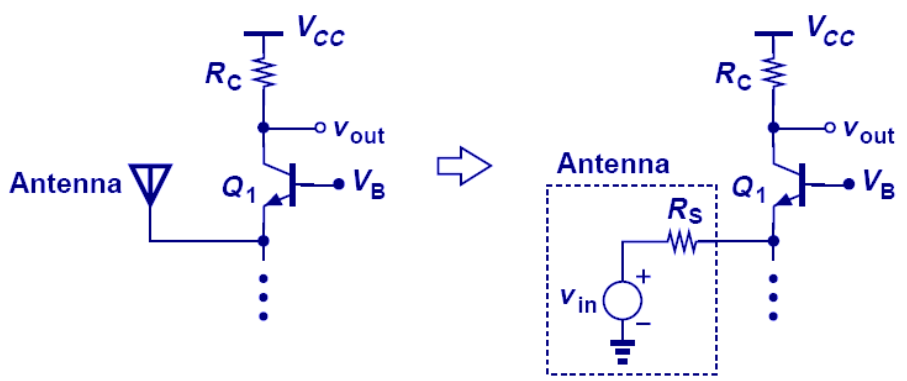

- An antenna usually has low output impedance; therefore, a correspondingly low input impedance is required for the following stage.