

Fundamentals of Microelectronics

- CH1 Why Microelectronics?
- CH2 Basic Physics of Semiconductors
- CH3 Diode Circuits
- CH4 Physics of Bipolar Transistors
- CH5 Bipolar Amplifiers
- CH6 Physics of MOS Transistors
- CH7 CMOS Amplifiers
- CH8 Operational Amplifier As A Black Box

1

Chapter 8 Operational Amplifier as A Black Box

- 8.1 General Considerations
- 8.2 Op-Amp-Based Circuits
- 8.3 Nonlinear Functions
- 8.4 Op-Amp Nonidealities
- 8.5 Design Examples




2

Chapter Outline

General Concepts	Linear Op Amp Circuits	Nonlinear Op Amp Circuits	Op Amp Nonidealities
<ul style="list-style-type: none"> • Op Amp Properties 	<ul style="list-style-type: none"> • Noninverting Amplifier • Inverting Amplifier • Inetgrator and Differentiator • Voltage Added 	<ul style="list-style-type: none"> • Precision Rectifier • Logarithmic Amplifier • Square Root Circuit 	<ul style="list-style-type: none"> • DC Offsets • Input Bias Currents • Speed Limitations • Finite Input and Output Impedances

CH8 Operational Amplifier as A Black Box
3

Basic Op Amp

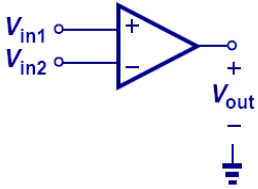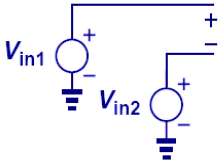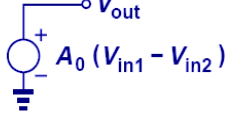
$$V_{out} = A_0(V_{in1} - V_{in2})$$

➤ **Op amp is a circuit that has two inputs and one output.**

➤ **It amplifies the difference between the two inputs.**

CH8 Operational Amplifier as A Black Box
4

Inverting and Non-inverting Op Amp

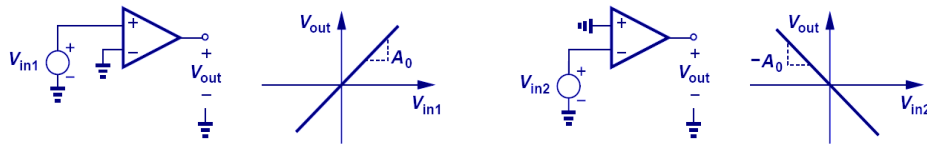

- If the negative input is grounded, the gain is positive.
- If the positive input is grounded, the gain is negative.

CH8 Operational Amplifier as A Black Box

5

Ideal Op Amp

- Infinite gain
- Infinite input impedance
- Zero output impedance
- Infinite speed

CH8 Operational Amplifier as A Black Box

6

Virtual Short

V_{in1} (+)
 V_{in2} (-)

➤ Due to infinite gain of op amp, the circuit forces V_{in2} to be close to V_{in1} , thus creating a virtual short.

CH8 Operational Amplifier as A Black Box 7


Unity Gain Amplifier

$$V_{out} = A_0 (V_{in} - V_{out})$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0}$$

CH8 Operational Amplifier as A Black Box 8

Op Amp with Supply Rails

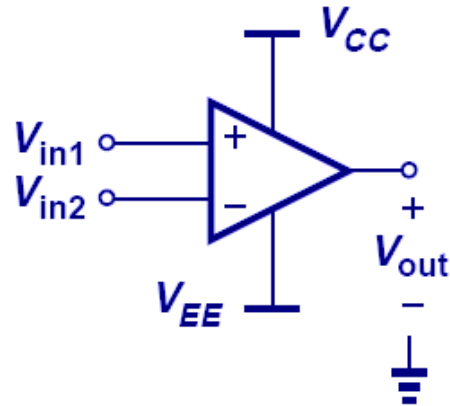


- To explicitly show the supply voltages, V_{CC} and V_{EE} are shown.
- In some cases, V_{EE} is zero.

CH8 Operational Amplifier as A Black Box

9

Noninverting Amplifier (Infinite A_0)

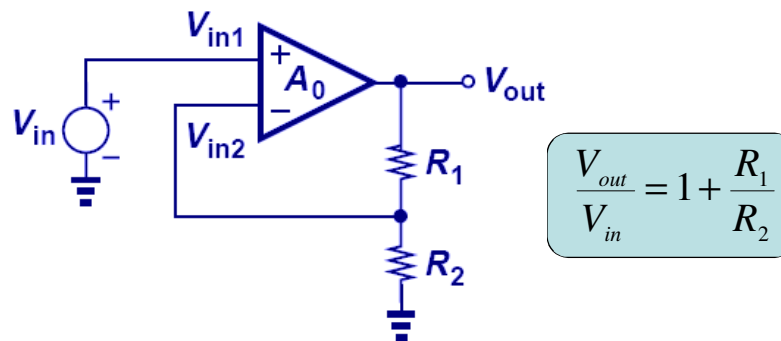


- A noninverting amplifier returns a fraction of output signal thru a resistor divider to the negative input.
- With a high A_0 , V_{out}/V_{in} depends only on ratio of resistors, which is very precise.

CH8 Operational Amplifier as A Black Box

10



Noninverting Amplifier (Finite A_0)

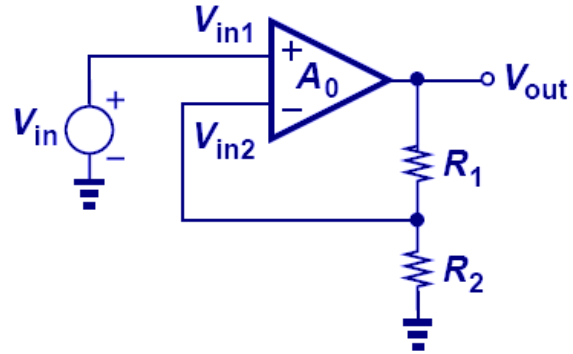

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left[1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0}\right]$$


➤ The error term indicates the larger the closed-loop gain, the less accurate the circuit becomes.

Extreme Cases of R_2 (Infinite A_0)

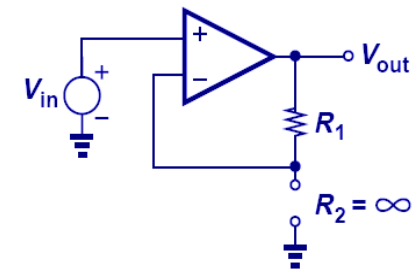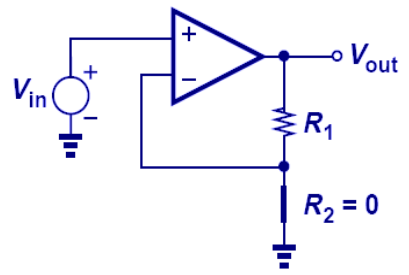


- If R_2 is zero, the loop is open and V_{out}/V_{in} is equal to the intrinsic gain of the op amp.
- If R_2 is infinite, the circuit becomes a unity-gain amplifier and V_{out}/V_{in} becomes equal to one.


Inverting Amplifier

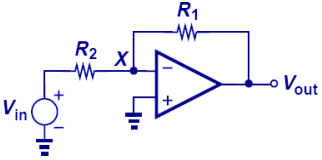

(a)

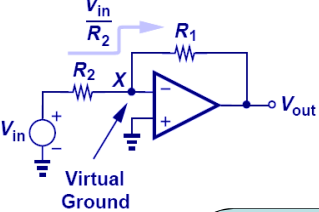

(b)



(c)


$$\frac{0 - V_{out}}{R_1} = \frac{V_{in}}{R_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{-R_1}{R_2}$$


➤ Infinite A_0 forces the negative input to be a virtual ground.

CH8 Operational Amplifier as A Black Box
13

Another View of Inverting Amplifier

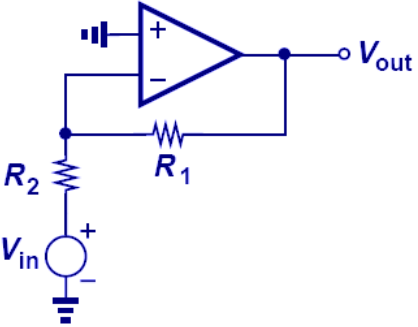


Inverting

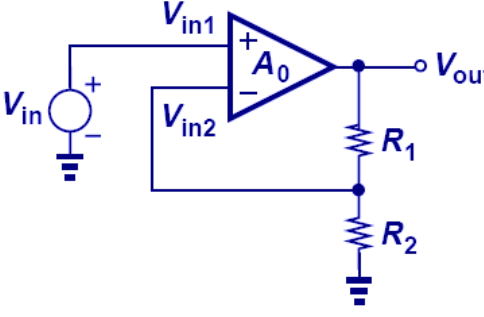

Noninverting

CH8 Operational Amplifier as A Black Box
14

Gain Error Due to Finite A_0

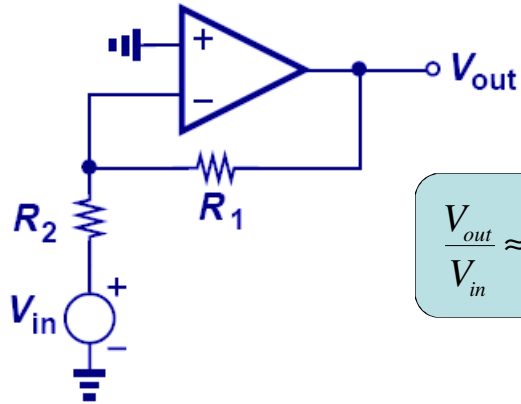


$$\frac{V_{out}}{V_{in}} \approx -\frac{R_1}{R_2} \left[1 - \frac{1}{A_0} \left(1 + \frac{R_1}{R_2} \right) \right]$$

➤ The larger the closed loop gain, the more inaccurate the circuit is.

CH8 Operational Amplifier as A Black Box

15

Complex Impedances Around the Op Amp

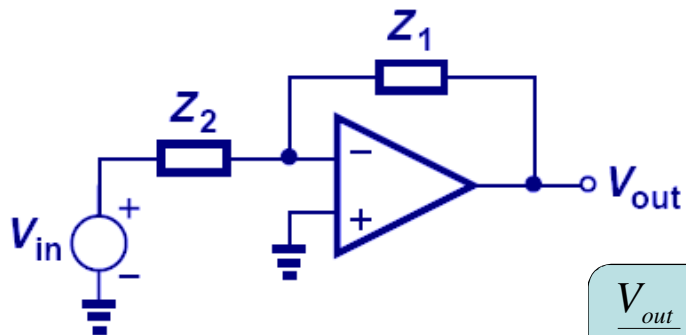

$$\frac{V_{out}}{V_{in}} \approx -\frac{Z_1}{Z_2}$$

➤ The closed-loop gain is still equal to the ratio of two impedances.

CH8 Operational Amplifier as A Black Box

16

Integrator

$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 C_1 s}$$

$$V_{out} = -\frac{1}{R_1 C_1} \int V_{in} dt$$


CH8 Operational Amplifier as A Black Box
17

Integrator with Pulse Input

$$V_{out} = -\frac{1}{R_1 C_1} \int V_{in} dt = -\frac{V_1}{R_1 C_1} t \quad 0 < t < T_b$$

CH8 Operational Amplifier as A Black Box
18

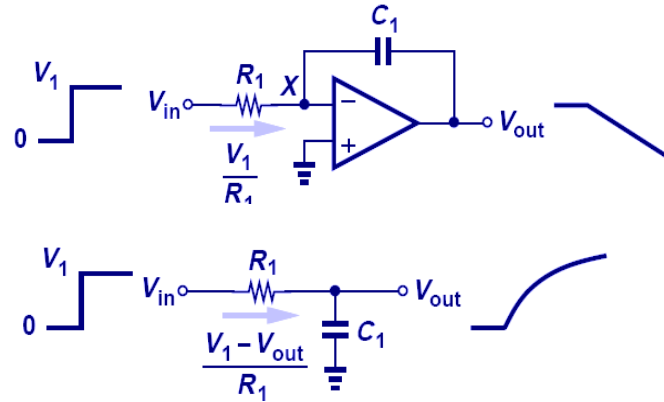Comparison of Integrator and RC Lowpass Filter




- The RC low-pass filter is actually a “passive” approximation to an integrator.
- With the RC time constant large enough, the RC filter output approaches a ramp.

CH8 Operational Amplifier as A Black Box

19

Lossy Integrator

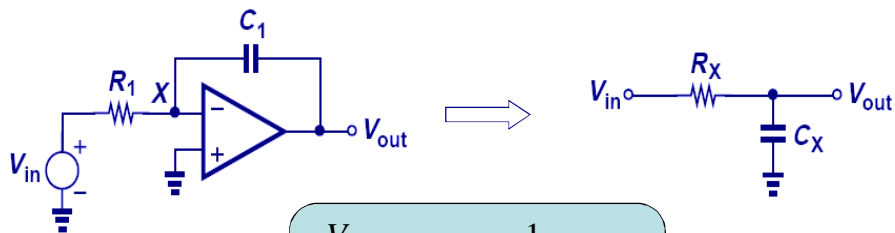


$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + \left(1 + \frac{1}{A_0}\right) R_1 C_1 s}$$


- When finite op amp gain is considered, the integrator becomes lossy as the pole moves from the origin to $-1/[(1+A_0)R_1C_1]$.
- It can be approximated as an RC circuit with C boosted by a factor of A_0+1 .

CH8 Operational Amplifier as A Black Box

20

Differentiator

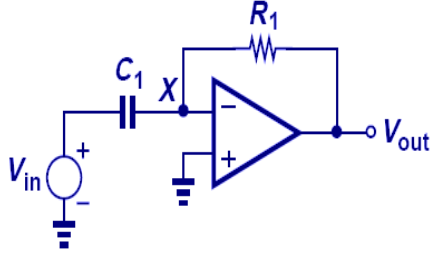

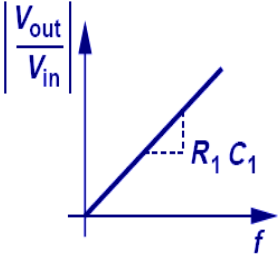



$$V_{out} = -R_1 C_1 \frac{dV_{in}}{dt}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_1}{\frac{1}{C_1 s}} = -R_1 C_1 s$$

CH8 Operational Amplifier as A Black Box
21

Differentiator with Pulse Input

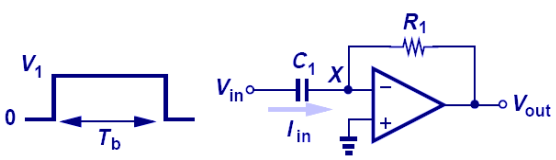


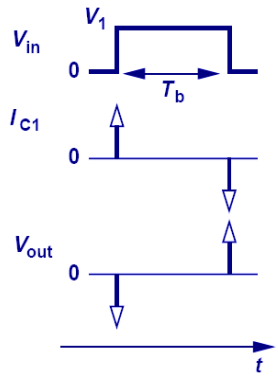

$$V_{out} = \mp R_1 C_1 V_1 \delta(t)$$

CH8 Operational Amplifier as A Black Box
22

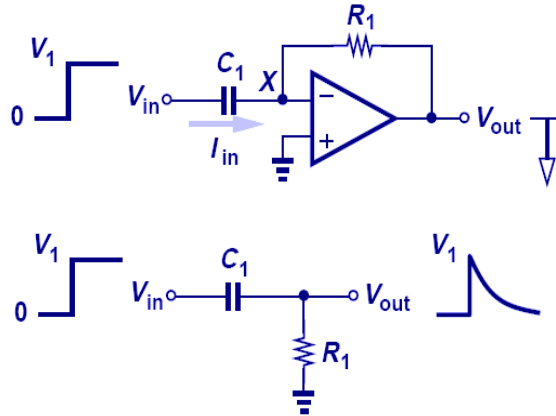Comparison of Differentiator and High-Pass Filter




- The RC high-pass filter is actually a passive approximation to the differentiator.
- When the RC time constant is small enough, the RC filter approximates a differentiator.

CH8 Operational Amplifier as A Black Box

23

Lossy Differentiator

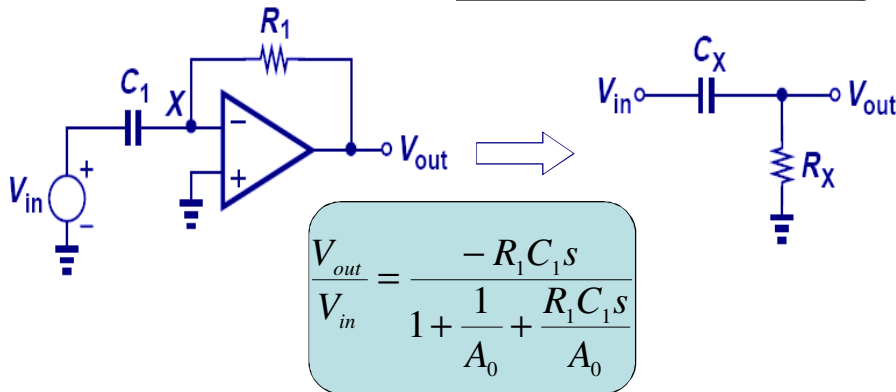


- When finite op amp gain is considered, the differentiator becomes lossy as the zero moves from the origin to $-(A_0+1)/R_1 C_1$.
- It can be approximated as an RC circuit with R reduced by a factor of (A_0+1) .

CH8 Operational Amplifier as A Black Box

24


Op Amp with General Impedances

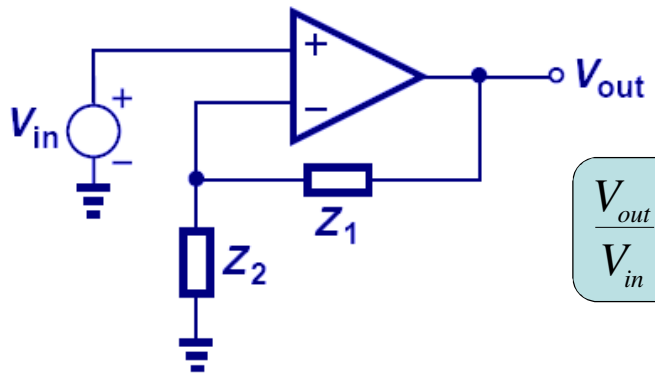

$$\frac{V_{out}}{V_{in}} = 1 + \frac{Z_1}{Z_2}$$

➤ This circuit cannot operate as ideal integrator or differentiator.

Voltage Adder

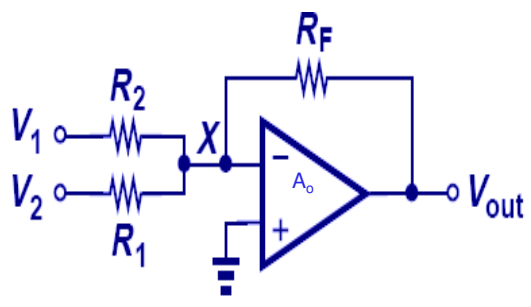

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$V_{out} = -\frac{R_F}{R} (V_1 + V_2)$$

If \$R_1 = R_2 = R\$

➤ If \$A_o\$ is infinite, X is pinned at ground, currents proportional to \$V_1\$ and \$V_2\$ will flow to X and then across \$R_F\$ to produce an output proportional to the sum of two voltages.

Precision Rectifier

Diagram (a): Op-amp with feedback resistor R_1 and input node X .

Diagram (b): Op-amp with feedback resistor R_1 , diode D_1 , and input node X .

Waveforms: V_{in} , V_Y (with $V_{D,on}$ level), and V_{out} vs t .

- When V_{in} is positive, the circuit in b) behaves like that in a), so the output follows input.
- When V_{in} is negative, the diode opens, and the output drops to zero. Thus performing rectification.

CH8 Operational Amplifier as A Black Box
27

Inverting Precision Rectifier


Diagram: Inverting op-amp with resistor R_1 , diode D_1 , and input node X .

Waveforms: V_{in} , V_X , V_Y (with $V_{D,on}$ level), and $V_{D,on}$ vs t .

- When V_{in} is positive, the diode is on, V_y is pinned around $V_{D,on}$, and V_x at virtual ground.
- When V_{in} is negative, the diode is off, V_y goes extremely negative, and V_x becomes equal to V_{in} .

CH8 Operational Amplifier as A Black Box
28

Logarithmic Amplifier

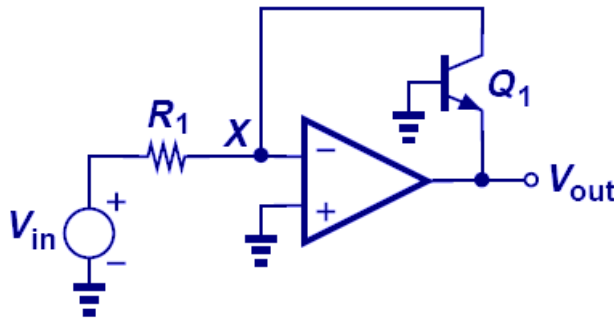


$$V_{out} = -V_T \ln \frac{V_{in}}{R_1 I_S}$$

- By inserting a bipolar transistor in the loop, an amplifier with logarithmic characteristic can be constructed.
- This is because the current to voltage conversion of a bipolar transistor is a natural logarithm.

CH8 Operational Amplifier as A Black Box

29

Square-Root Amplifier

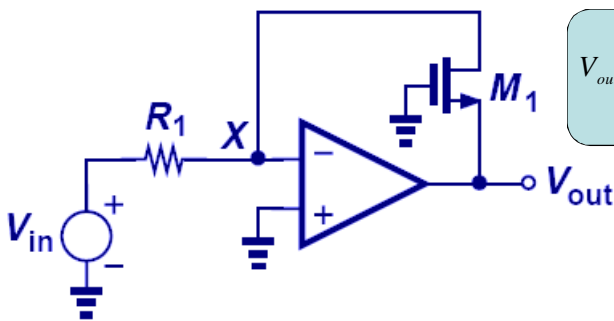




$$V_{out} = - \sqrt{\frac{2V_{in}}{\mu_n C_{ox} \frac{W}{L} R_1}} - V_{TH}$$

- By replacing the bipolar transistor with a MOSFET, an amplifier with a square-root characteristic can be built.
- This is because the current to voltage conversion of a MOSFET is square-root.

CH8 Operational Amplifier as A Black Box

30


Op Amp Nonidealities: DC Offsets

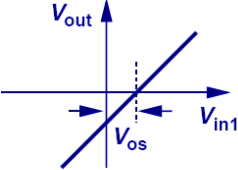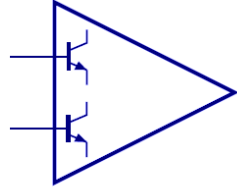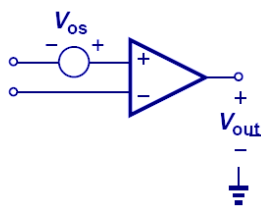➤ Offsets in an op amp that arise from input stage mismatch cause the input-output characteristic to shift in either the positive or negative direction (the plot displays positive direction).

CH8 Operational Amplifier as A Black Box 31

Effects of DC Offsets

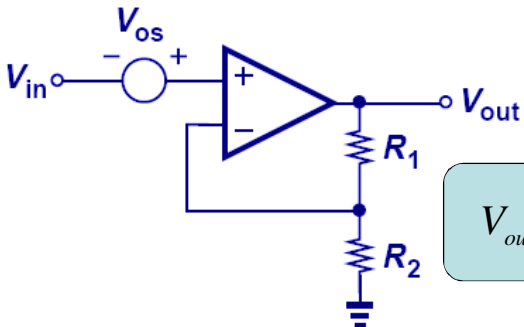


$$V_{out} = \left(1 + \frac{R_1}{R_2}\right)(V_{in} + V_{os})$$

➤ As it can be seen, the op amp amplifies the input as well as the offset, thus creating errors.



CH8 Operational Amplifier as A Black Box 32

Saturation Due to DC Offsets


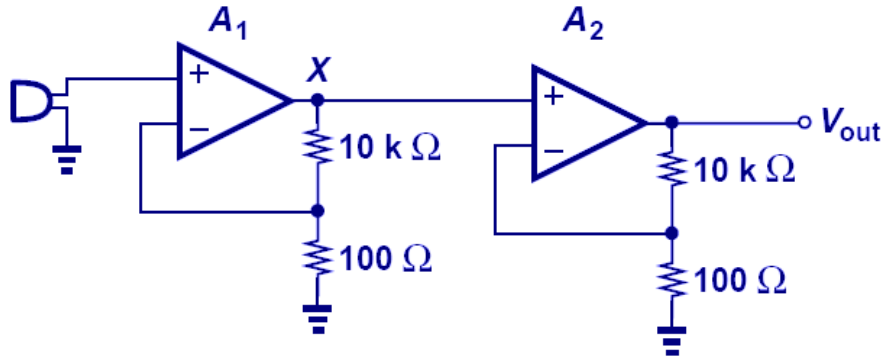


➤ Since the offset will be amplified just like the input signal, output of the first stage may drive the second stage into saturation.

Offset in Integrator

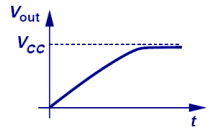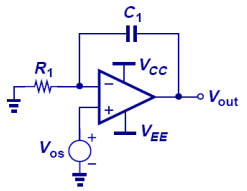
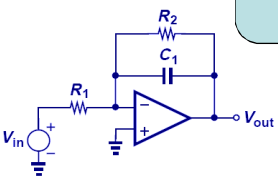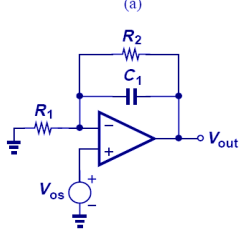
$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \frac{1}{R_2 C_1 s + 1}$$



➤ A resistor can be placed in parallel with the capacitor to “absorb” the offset. However, this means the closed-loop transfer function no longer has a pole at origin.

Input Bias Current

V_{in1} V_{in2} I_{B1} I_{B2} V_{out}

➤ The effect of bipolar base currents can be modeled as current sources tied from the input to ground.

CH8 Operational Amplifier as A Black Box 35

Effects of Input Bias Current on Noninverting Amplifier

(a)

(b)

(c)

$$V_{out} = -R_2 I_{B2} \left(-\frac{R_1}{R_2} \right) = R_1 I_{B2}$$

➤ It turns out that I_{B1} has no effect on the output and I_{B2} affects the output by producing a voltage drop across R_1 .

CH8 Operational Amplifier as A Black Box 36

Input Bias Current Cancellation

$$V_{out} = V_{corr} \left(1 + \frac{R_1}{R_2} \right) + I_{B2} R_1$$

- We can cancel the effect of input bias current by inserting a correction voltage in series with the positive terminal.
- In order to produce a zero output, $V_{corr} = -I_{B2}(R_1 || R_2)$.

CH8 Operational Amplifier as A Black Box 37


Correction for β Variation

$$I_{B1} = I_{B2}$$

- Since the correction voltage is dependent upon β , and β varies with process, we insert a parallel resistor combination in series with the positive input. As long as $I_{B1} = I_{B2}$, the correction voltage can track the β variation.

CH8 Operational Amplifier as A Black Box 38

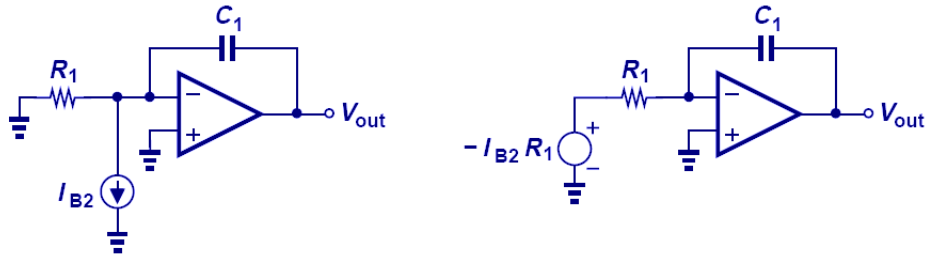
Effects of Input Bias Currents on Integrator



$$V_{out} = -\frac{1}{R_1 C_1} \int (-I_{B2} R_1) dt$$


➤ Input bias current will be integrated by the integrator and eventually saturate the amplifier.

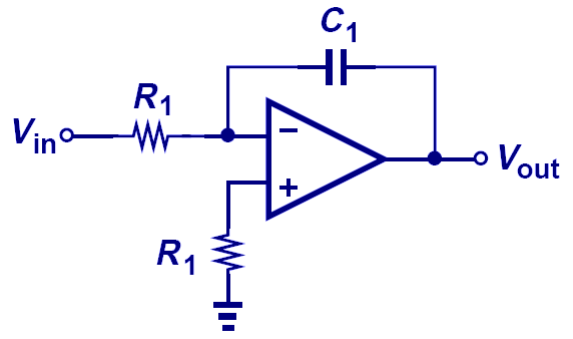Integrator's Input Bias Current Cancellation



➤ By placing a resistor in series with the positive input, integrator input bias current can be cancelled.
 ➤ However, the output still saturates due to other effects such as input mismatch, etc.

Speed Limitation

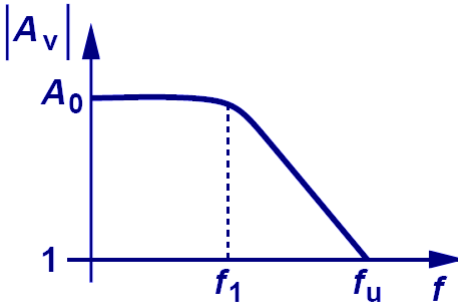


$$\frac{V_{out}}{V_{in1} - V_{in2}}(s) = \frac{A_0}{1 + \frac{s}{\omega_1}}$$

➤ Due to internal capacitances, the gain of op amps begins to roll off.

CH8 Operational Amplifier as A Black Box
41




Bandwidth and Gain Tradeoff

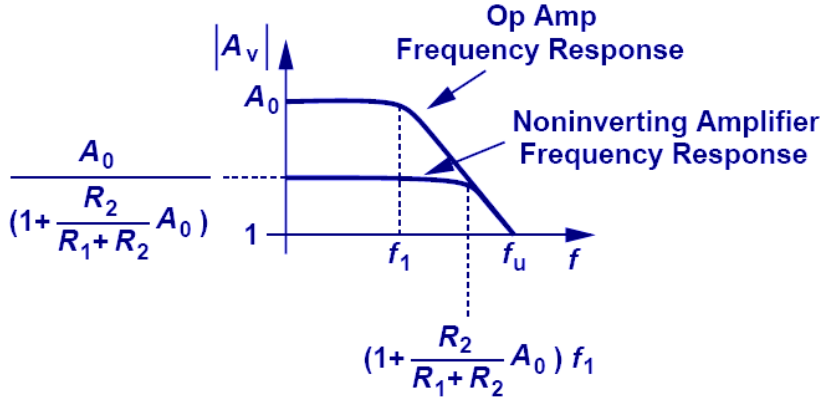

➤ Having a loop around the op amp (inverting, noninverting, etc) helps to increase its bandwidth. However, it also decreases the low frequency gain.

CH8 Operational Amplifier as A Black Box
42


Slew Rate of Op Amp

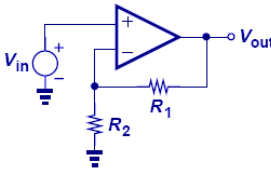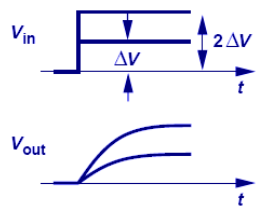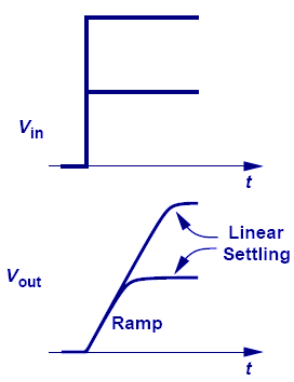- In the linear region, when the input doubles, the output and the output slope also double. However, when the input is large, the op amp slews so the output slope is fixed by a constant current source charging a capacitor.
- This further limits the speed of the op amp.

CH8 Operational Amplifier as A Black Box
43

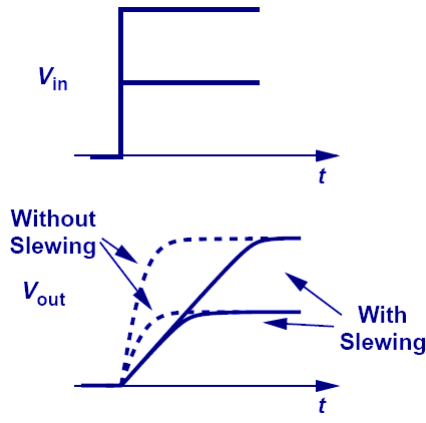
Comparison of Settling with and without Slew Rate




- As it can be seen, the settling speed is faster without slew rate (as determined by the closed-loop time constant).

CH8 Operational Amplifier as A Black Box
44


Slew Rate Limit on Sinusoidal Signals

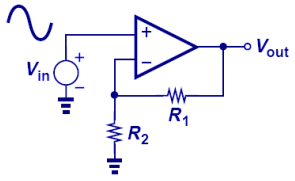

(a)

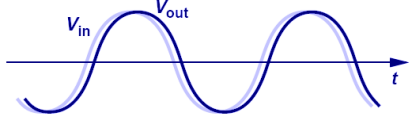

(b)

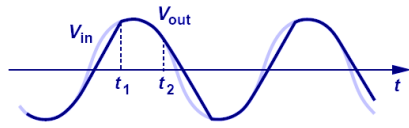


(c)


$$\frac{dV_{out}}{dt} = V_0 \left(1 + \frac{R_1}{R_2} \right) \omega \cos \omega t$$

- As long as the output slope is less than the slew rate, the op amp can avoid slewing.
- However, as operating frequency and/or amplitude is increased, the slew rate becomes insufficient and the output becomes distorted.

CH8 Operational Amplifier as A Black Box
45

Maximum Op Amp Swing

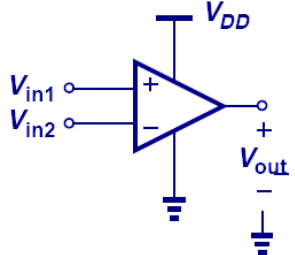

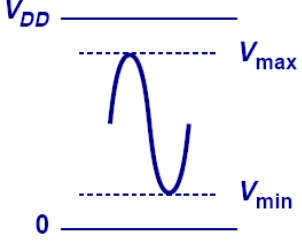


$$V_{out} = \frac{V_{max} - V_{min}}{2} \sin \omega t + \frac{V_{max} + V_{min}}{2} \quad \omega_{FP} = \frac{SR}{\frac{V_{max} - V_{min}}{2}}$$

- To determine the maximum frequency before op amp slews, first determine the maximum swing the op amp can have and divide the slew rate by it.

CH8 Operational Amplifier as A Black Box
46

Nonzero Output Resistance

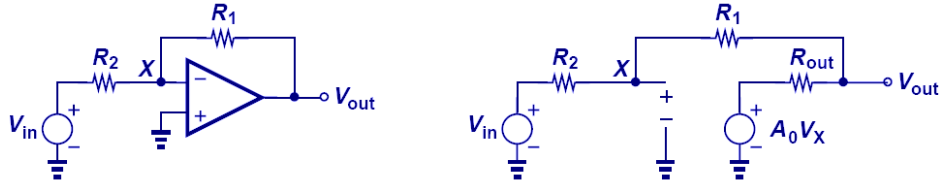

$$\frac{v_{out}}{v_{in}} = -\frac{R_1}{R_2} \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}}$$

- In practical op amps, the output resistance is not zero.
- It can be seen from the closed loop gain that the nonzero output resistance increases the gain error.

CH8 Operational Amplifier as A Black Box

47

Design Examples

- Many design problems are presented at the end of the chapter to study the effects of finite loop gain, restrictions on peak to peak swing to avoid slewing, and how to design for a certain gain error.

CH8 Operational Amplifier as A Black Box

48